
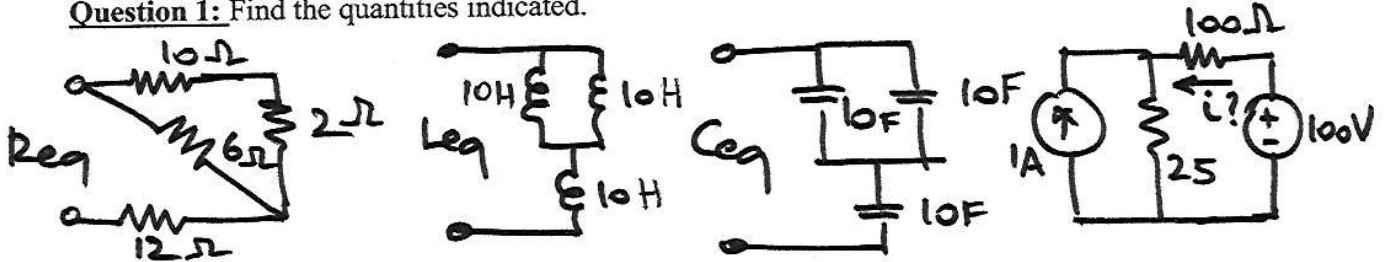


Please note: We cannot read your work carefully unless you write it carefully. Answers without a clear derivation will receive zero credit.


**Question 1:** Find the quantities indicated.

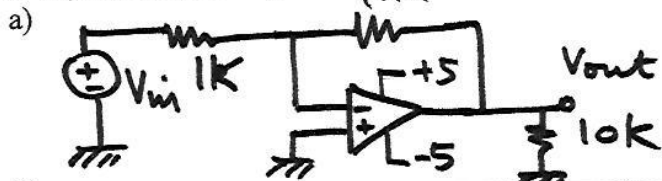

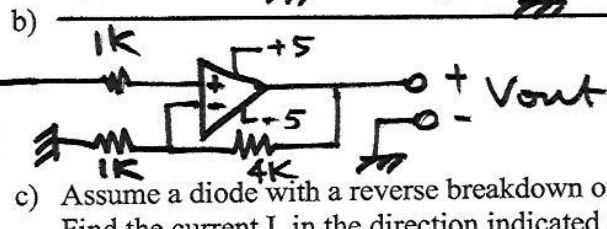**Question 2:** Find the quantities indicated. Assume opamps with very large gain in their linear region for a) and b).





$V_{in} = 0V \rightarrow V_{out} = ?$   
 $V_{in} = 0.2V \rightarrow V_{out} = ?$   
 $V_{in} = -5V \rightarrow V_{out} = ?$




$V_{in}(t) = 0.01 \sin(500t)$   
 $V_{out}(t) = \dots \dots \dots$   
 expansion

c) Assume a diode with a reverse breakdown of -10V and a forward voltage of 0.7V. Find the current I in the direction indicated for both cases.

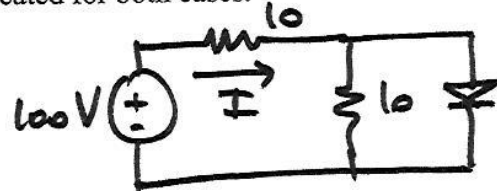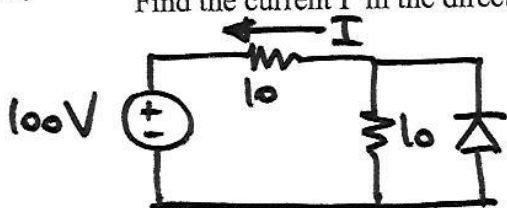

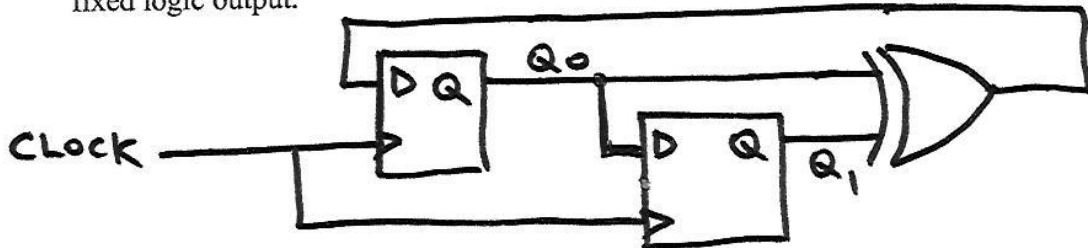**Question 3:**

- Plot the logic signals Q0 and Q1 for the flip-flop circuit shown below. The flip flops are positive clock edge triggered D flip-flops. The initial state of Q0 is high and the initial state of Q1 is low.
- Indicate if this circuit exhibits a repeating pattern at its output or settles into a fixed logic output.




**Question 4:** You are hired by the Metropolitan Transit Authority to design a speed limiting device for their city buses. Safety studies have shown that the bus speed should be limited to 50 miles/hour at all times. During the night however, a stricter speed limit of 30 miles/hour needs to be observed. When it is raining, the daytime speed limit reduces to 30 miles/hour and the night time limit to 20 miles/hour.

Your device receives two logic inputs: input line N is high if it is nighttime; input line R is high if it is raining. Your device has three outputs: line F goes high when the speed limit is 50 miles/hour; similarly lines TH and TW indicate speed limits of 30 and 20 miles/hour respectively. At all times *only one* of the outputs can be logic high.


- Make a truth table for the three output signals as a function of the two inputs.
- Write out the sum-of-products realization for each output. Verify if you can do any simplifications.
- Make a logic circuit using 2 input NAND gates only. Try to use as few NAND gates as possible.

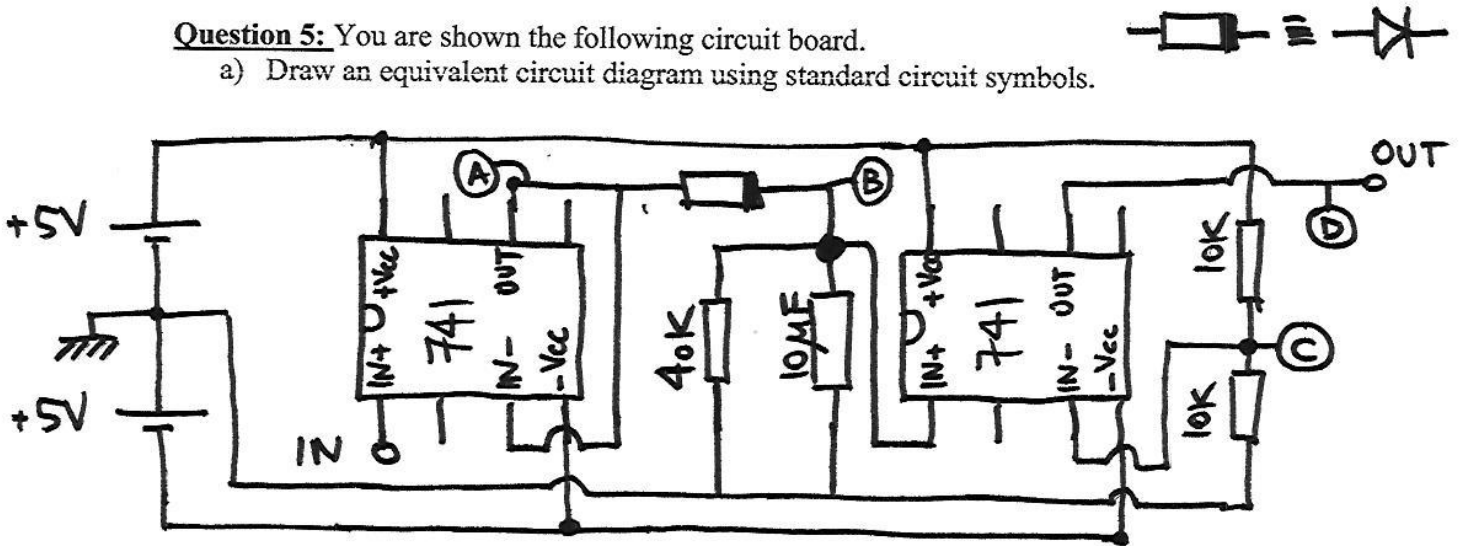**Question 5:** You are shown the following circuit board.

- Draw an equivalent circuit diagram using standard circuit symbols.





- Assume the diode is ideal and the opamps have a very large gain in their linear region. You apply the following signal at the input of the circuit. Plot the waveforms at the points A, B, C, and D in the circuit for the shown input signal. *with respect to ground. The capacitor is initially discharged.*

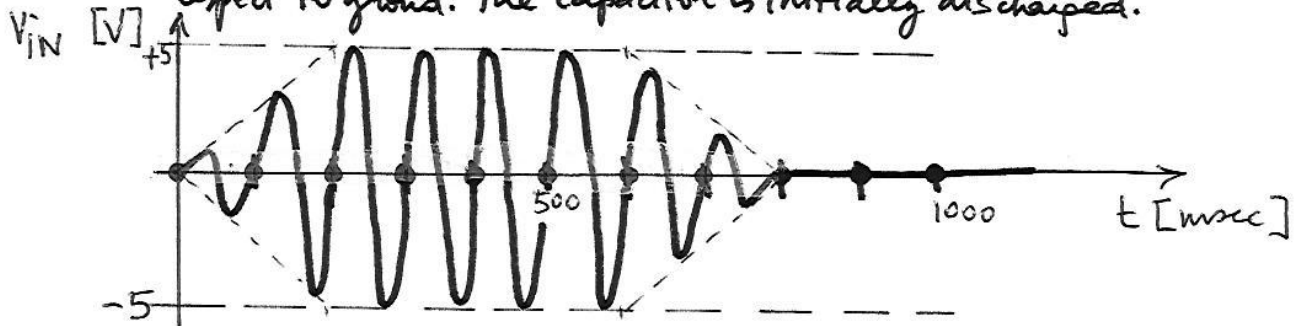

**Question 6:** You are asked to design a logic inverter using the circuit shown below with an nMOS transistor and a resistor. The transistor characteristics are given below.


- Find the appropriate value of the resistance  $R$  so that  $V_{out} > 6.5V$  when  $V_{in}=0$  and  $V_{out} < 2V$  when  $V_{in}=7V$ .
- For your choice of  $R$ , plot  $V_{out}$  as a function of  $V_{in}$ , for  $V_{in}: 0 \rightarrow 7V$ . If you are not able to solve part a), clearly indicate so, and use a resistance value of  $2\text{ K}$  for this part.

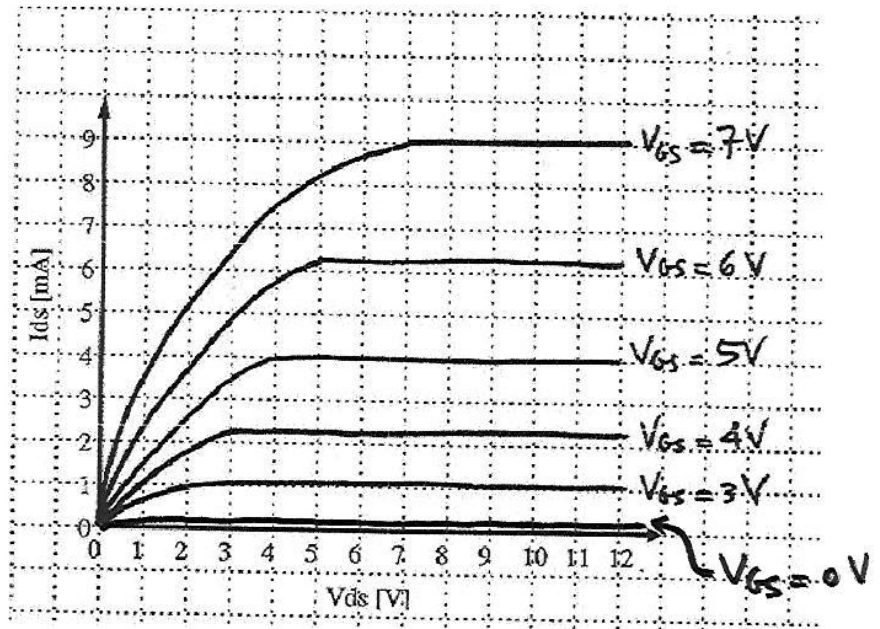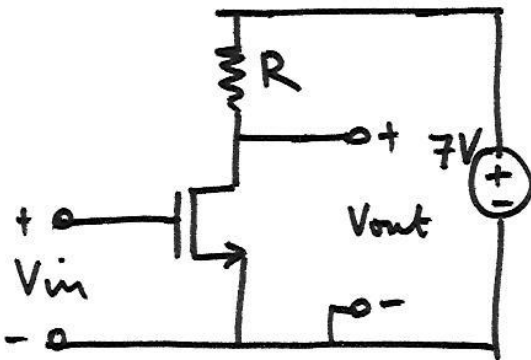

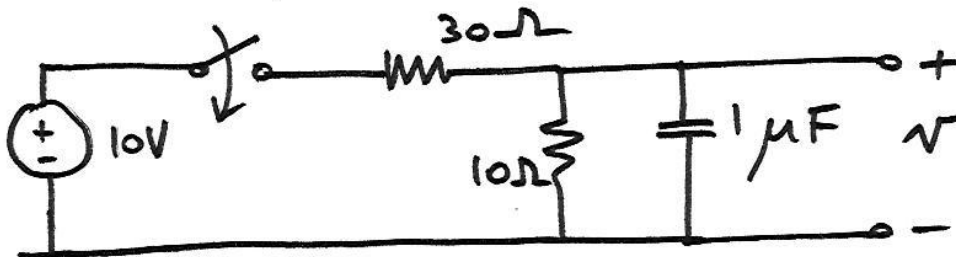**Question 7:** The switch in the circuit below has been open for a very long time. At time  $t=10\text{sec}$  the switch closes.

- Find the DC steady state voltage  $V$  when the switch is open
- Find the DC steady state voltage  $V$  when the switch is closed
- Find the expression for  $V(t)$  valid for  $t: 0 \rightarrow +\infty$
- Plot  $V(t)$  as a function of time. Indicate interesting points

**Remark:** Remember you can (but you do not have to) apply Thevenin/Norton source transformations if you feel this simplifies the problem. Or, if you prefer you can write out the differential equation for  $V$ .



*✂* END

Good luck!