

1) (a) DC Bias point

Voltage at B $\rightarrow 5k\Omega \times 100\mu A = 0.5V$ [3]

Resulting voltage at A $\rightarrow \frac{100\mu A}{2} \times 50 \times (V_A - 0.5 - 0.5)^2$
 $\approx 100\mu A$ [neglecting effect]
 $\Rightarrow V_A = \underline{1.2 \text{ Volts}}$ of V_{DS}

(We can use the above equation because [3]
 M_1 is diode connected. $\therefore V_{GS} = V_{DS}$. $\therefore V_{DS} > V_{GS} - V_T$)
 $\therefore M_1$ is in saturation.

This is a current mirror. So the same $100\mu A$ current flows through M_1, M_2 (if M_1 is in saturation)

\Rightarrow voltage at C = $100\mu A \times 5k\Omega = 0.5 \text{ Volts}$. [3]

M_2 could be in saturation or linear. Let's try to find out where.

If M_2 in sat : $I_D = \frac{50\mu A}{2} \times 1 \times 2.0^2 \times \left(1 + \frac{V_{DS2}}{V_A}\right)$ ← for pmos
 $= \frac{100\mu A}{2} \times 50 \times 0.2^2 \times \left(1 + \frac{V_{DS1}}{V_A}\right)$ ← for nmos

or $V_{DS2} = V_{DS1}$

But $V_{DS2} + V_{DS1} = 2.5V$. $\therefore V_{DS2} = V_{DS1} = 1.25V$.

Is ~~that~~ M_2 in sat? For M_2 , $1.25 > 2.5 - 0.5$

So the above derivation is not valid.

If M_2 in linear: $I_D = 50 \mu A \times 2.0 \times V_{DS} = 100 \mu A$

$\therefore V_{DS} = 1 \text{ Volt}$

Is M_2 in linear? For M_2 , $1 < 2.5 - 0.5$.

So M_2 is in linear region — and $V_D = 2.0 \text{ Volts}$

[4]


(b) $M_1 \rightarrow$ saturation, strong inv.

$M_2 \rightarrow$ non-saturation, strong inv.

$M_3 \rightarrow$ saturation, ~~linear~~ strong inv.

[3]

(c) For any transistor M_1, M_2, M_3 :

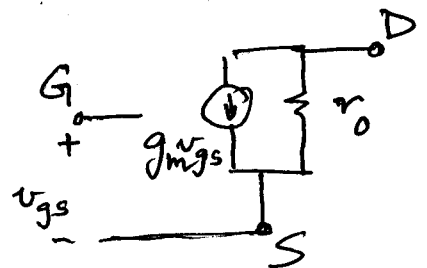

For M_1, M_3 (sat, strong inv)

$g_{m1} \approx \mu C_{ox} \frac{W}{L} (V_{GS} - V_T) = 100 \times 50 \times 0.2 \mu S = \underline{1 \text{ mS}}$

$g_{ds1} = I_D / V_A = \frac{100 \mu A}{10 V} = 10 \mu S$

for M_2 (non-sat, strong inv)


$$g_{m2} = \mu C_{ox} \frac{W}{L} V_{DS} = 50 \times 1 \times 1 \mu S = 50 \mu S$$

$$g_{ds2} = \mu C_{ox} \frac{W}{L} (V_{GS} - V_T) = 50 \times 1 \times 2 \mu S = 100 \mu S$$

[4]

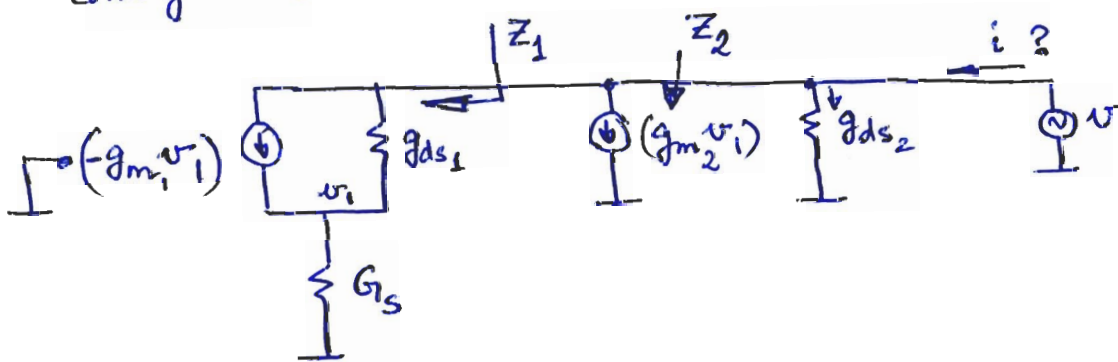2) Small signal output impedance

Apply small signal voltage at output, short input to 0, find current coming in:



[Note: Gate/drain of M_3 has a small signal voltage of 0 — always. This is because there is a constant bias current through M_3 . Convince yourselves about this.]

~~Straight forward "brute force" approach~~

We do KCL at node v_1 :

$$v_1 G_S = -v_1 g_{m1} + (v - v_1) g_{ds1}$$

$$\therefore v_1 (G_S + g_{m1} + g_{ds1}) = v \cdot g_{ds1}$$

$$\therefore v_1 = \frac{g_{ds1}}{G_S + g_{m1} + g_{ds1}} v$$

Straight forward "Brute force" Approach

Now $i = v_1 \cdot G_S + g_{m2} v_1 + g_{ds2} v$

$$= v \cdot g_{ds2} + v \cdot \frac{(g_{m2} + G_S) g_{ds1}}{G_S + g_{m1} + g_{ds1}} \Rightarrow G_{out} = g_{ds2} + \frac{(g_{m2} + G_S) g_{ds1}}{G_S + g_{m1} + g_{ds1}}$$

⇒ Plug in the values for g_{m1} , g_{m2} , g_{ds1} , g_{ds2}

$$R_{out} = \frac{1}{G_{out}} = \underline{\underline{9.797 \text{ k}\Omega}}$$

[10]

Alternative method :-

Looking into Z_1 , we see a ~~cascade~~ device with source degeneration of G_S .

$$Z_1 = Z_{out}(\text{source degeneration}) = r_{o1} + R_S + g_{m1} r_{o1} R_S$$

For M_2 , we see a current of $g_{m2} v_1 + g_{ds2} v$

$$= \left(\frac{g_{m2} g_{ds1}}{G_S + g_{m1} + g_{ds1}} + g_{ds2} \right) v$$

$$\text{or } Z_2 = \frac{1}{\frac{g_{m2} g_{ds1}}{G_S + g_{m1} + g_{ds1}} + g_{ds2}}$$

$$\therefore \frac{1}{Z_{out}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$= \frac{1}{r_{o1} + R_S + g_{m1} r_{o1} R_S} + \left(\frac{g_{m2} g_{ds1}}{G_S + g_{m1} + g_{ds1}} + g_{ds2} \right)$$


$$= \frac{G_S g_{ds1}}{G_S + g_{ds1} + g_{m1}} + \frac{g_{m2} g_{ds1}}{G_S + g_{m1} + g_{ds1}} + g_{ds2}$$

$$= g_{ds2} + \frac{(g_{m2} + G_S) g_{ds1}}{G_S + g_{m1} + g_{ds1}} \Rightarrow R_{out} = \underline{\underline{9.797 \text{ k}\Omega}}$$

(same expression as before)

2) Small Signal Gain :

"Brute force" method :

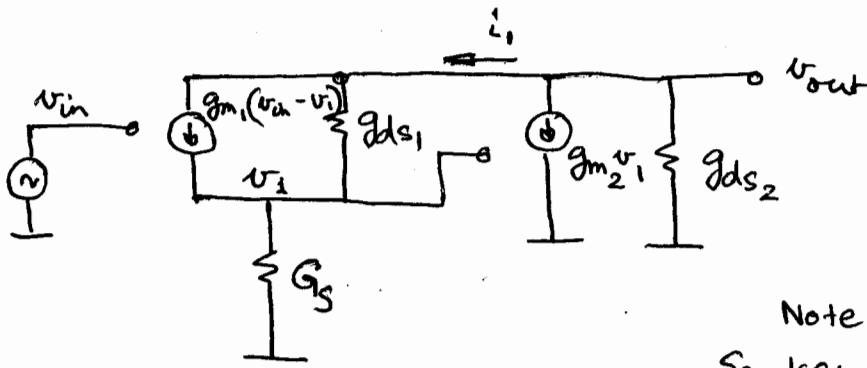

Note that $i_1 = v_1 G_S$.

So KCL at $v_{out} \Rightarrow$

$$v_1 (G_S + g_{m2}) = -v_{out} g_{ds2}$$

$$\text{or } v_1 = -v_{out} \cdot \frac{g_{ds2}}{G_S + g_{m2}} \quad \text{--- (1)}$$

~~KCL for v_{out}~~ $v_1 (G_S + g_{m2}) =$

$$\text{KCL for } v_1 : g_{m1}(v_{in} - v_1) + g_{ds1}(v_{out} - v_1) = v_1 G_S$$

$$\text{or } g_{m1} v_{in} = -g_{ds1} v_{out} + v_1 (G_S + g_{ds1} + g_{m1})$$



$$= -v_{out} \left(g_{ds1} + \frac{g_{ds2}}{G_S + g_{m2}} (G_S + g_{ds1} + g_{m1}) \right)$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = - \frac{g_{m1} (G_S + g_{m2})}{g_{ds1} (G_S + g_{m2}) + g_{ds2} (G_S + g_{ds1} + g_{m1})}$$

$$\text{Plug in values } \Rightarrow \text{Gain} = \underline{\underline{-2.024}} \quad [10]$$

Another approach, using already computed R_{out} :

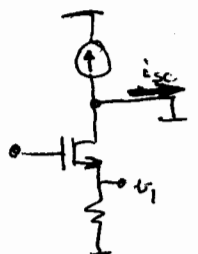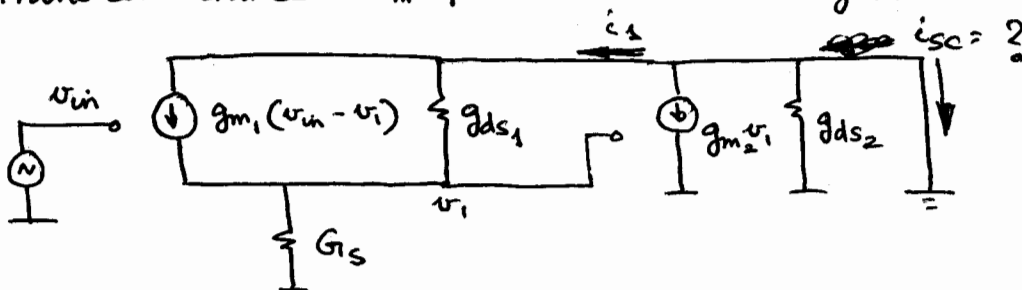Short output to ground and measure short circuit current \rightarrow This will give trans conductance G_m for the circuit \rightarrow gain will be $G_m R_{out}$



In this case $i_1 = v_1 G_S$.

$$-i_{sc} = i_1 + g_{m2} v_1 = (G_S + g_{m2}) v_1.$$


Note that v_1 is the voltage at the source of a source follower.

$$\text{So } v_1 = \frac{1/(G_S + g_{ds1})}{1/g_{m1} + 1/(G_S + g_{ds1})} \times v_{in} = \frac{g_{m1}}{g_{m1} + g_{ds1} + G_S} \cdot v_{in}$$


$$\text{So } i_{sc} = - \frac{g_{m1} (G_S + g_{m2})}{g_{m1} + g_{ds1} + G_S} \cdot v_{in}$$

$$\Rightarrow G_m = -206.61 \mu S$$
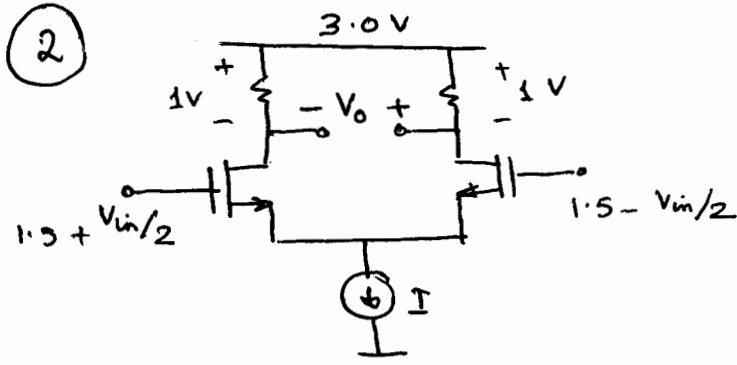
$$\therefore \text{gain} = G_m R_{out} = \underline{\underline{-2.024}}$$




Small signal \Rightarrow

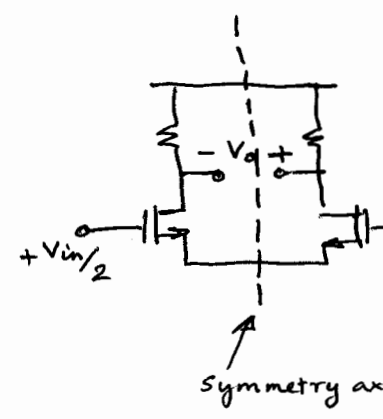

In small signal, take half of the circuit

(You can do this only when the circuit is completely symmetric.)

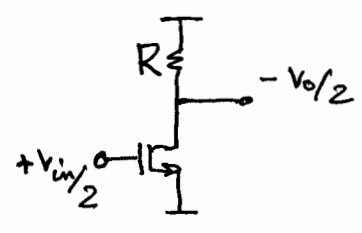Since one side has $+V_{in}/2$ and the other $-V_{in}/2$, there will be a "null" through the axis of symmetry on the circuit. This means that the source voltage will be at virtual ground and you will have $-V_o/2$ and $+V_o/2$ at the drain node.)



$$\rightarrow -V_o/2 = -g_m V_{in}/2 \cdot R$$

$$\therefore V_o/V_{in} = g_m \cdot R$$

(a) Assume the device is in strong inversion. Good assumption since $V_{GS} - V_T = 200\text{mV}$

$$g_m = \frac{2I_D}{V_{GS} - V_T}$$


$$= \frac{2I_D}{200\text{mV}}$$

$$\text{Gain} = g_m \cdot R = \frac{2I_D R}{200\text{mV}}$$

$$I_D \cdot R = 1\text{ Volt}$$

$$= \frac{2\text{V}}{200\text{mV}} = \underline{\underline{10}} \quad [10]$$

(b)

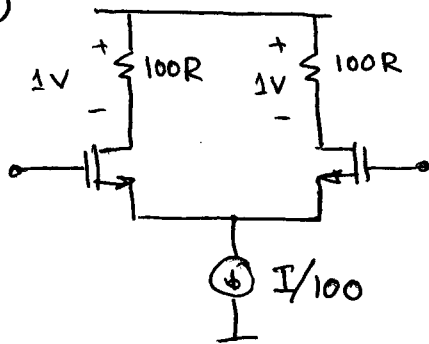

Here the current through drain is $100\times$ less than before.

For the same device, $100\times$ lesser current, V_{GS} will have to be much lesser.

For $I/2$, $V_{GS} - V_T = 200\text{ mV}$. $I_D \propto (V_{GS} - V_T)^2$.

If the same law holds, For $I/200$, $V_{GS} - V_T = 20\text{ mV}$.

↓
We know that at these voltages, the square law does not hold.

So is it in moderate inversion or weak inversion ?? Investigate further.

$I_2 = 2k n \phi_t^2$. In strong inv, $I_D = k/2 (V_{GS} - V_T)^2$.

For current I_2 (prev. case) $V_{GS} - V_T = 200\text{ mV}$, $I_D = k/2 \times 0.04$.
 $I_2 \approx 2k \times 1 \times 0.3^2$ } inv. coeff ≈ 10

$100\times$ less current means inv. coeff is also $100\times$ less.

So $I_D/I_2 \approx 0.1$. \leftarrow inv. coeff for this case \Rightarrow this is in weak inversion.


In weak inversion, $g_m = I_D / n \phi_t = 40 I_D$.

Gain = $g_m \cdot 100R$
 $= 40 \times 100 \times I_D \cdot R = 4000 \times I_D \cdot R$

$I_D \cdot 100R = 1\text{ Volt}$.


\therefore Gain = $40 \times (I_D \cdot 100R) = \underline{\underline{40}}$.

[10]

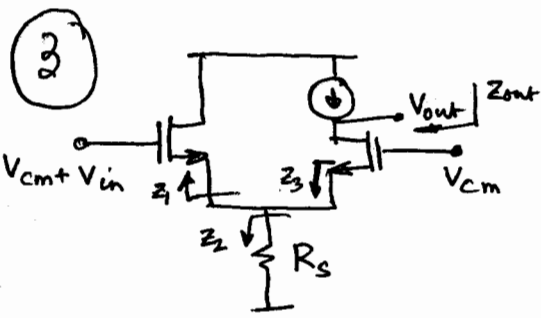

This circuit has no symmetry.
You cannot break into any half circuit.

Small signal picture :-

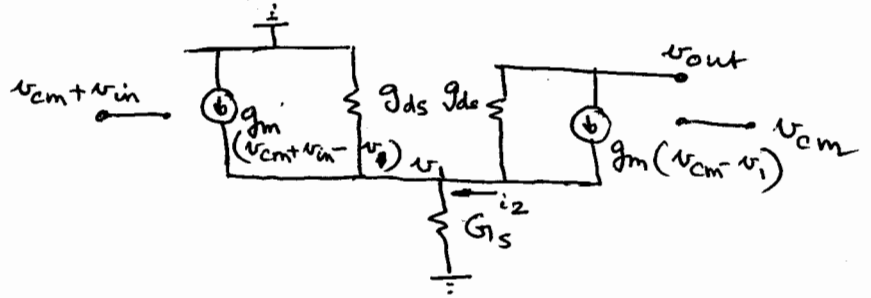

(1) v_o/v_{cm} : "Brute force" method :

Set $v_{in} = 0$. KCL at $v_i \Rightarrow v_i G_s = g_m(v_{cm} - v_i) - v_i g_{ds}$.

Note : current $i_2 = 0$ since the output is open!

$$\therefore v_i = v_{cm} \cdot \frac{g_m}{g_m + g_{ds} + G_s}$$

$$v_{out} = v_i - g_m(v_{cm} - v_i)/g_{ds}$$

$$= v_i (1 + g_m/g_{ds}) - g_m/g_{ds} v_{cm}$$

$$= v_{cm} \left[\frac{g_m}{g_m + g_{ds} + G_s} \cdot \frac{g_{ds} + g_m}{g_{ds}} - \frac{g_m}{g_{ds}} \right]$$

$$= v_{cm} \cdot \frac{g_m}{g_{ds}} \left[\frac{g_m + g_{ds}}{g_m + g_{ds} + G_s} - 1 \right] = -v_{cm} \cdot \frac{g_m}{g_{ds}} \cdot \frac{G_s}{g_m + g_{ds} + G_s}$$

$$\therefore \frac{v_{out}}{v_{cm}} = - \frac{g_m}{g_{ds}} \cdot \frac{G_s}{g_m + g_{ds} + G_s}$$

$$1/g_{ds} = 10 \text{ k}\Omega, \quad 1/G_s = 5 \text{ k}\Omega, \quad g_m = 2 \text{ mS}$$


$$\Rightarrow v_o/v_{cm} = \underline{\underline{-1.739}}$$

[15]

More intuitive approach

Compute Z_1 : Looking in from source

$$Z_1 = \frac{1}{g_m + g_{ds}}$$

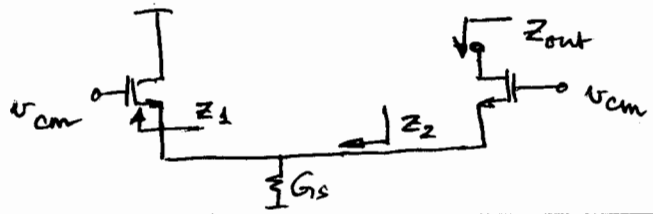

Compute Z_2 : $Z_2 = Z_1 \parallel R_S = \frac{1}{g_m + g_{ds} + G_S}$


Compute Z_{out} : (source follower)

$$Z_{out} = g_m \cdot Z_2 \cdot r_o + r_o + Z_2$$


$$= (1 + g_m/g_{ds}) Z_2 + 1/g_{ds} \Rightarrow 19.13 \text{ k}\Omega$$

[This Z_{out} will be used in the second part too]

Now measure short circuit current:

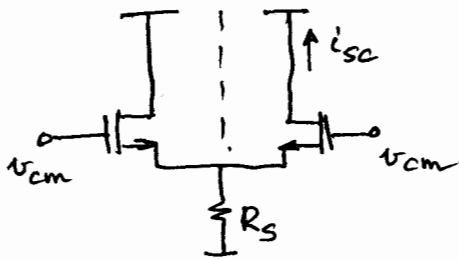

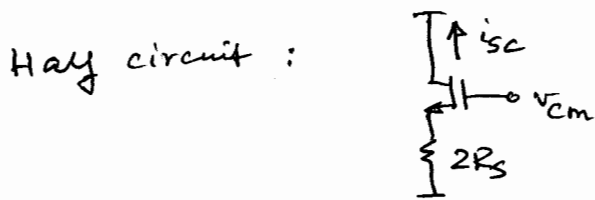Now, indeed this is symmetric. Break R_S into two parallel resistors of value $2R_S$. Let us break this along the dotted line. Since both sides are excited identically by v_{cm} , there will be an "open" along the symmetry axis.



Here, $i_{sc} = -\frac{v_{cm}}{2R_S} \times \text{gain of source follower}$

$$= -\frac{v_{cm}}{2R_S} \times \frac{(2R_S) \parallel r_o}{(2R_S) \parallel r_o + 1/g_m}$$

$$\Rightarrow G_{m_{cm}} = -90.9 \mu\text{S}$$

$\therefore v_{out}/v_{cm} = G_{m_{cm}} \cdot Z_{out} = \underline{\underline{-1.739}}$

(2) "Brute force"


set $v_{cm} = 0$. $v_i = v_{in} \cdot \frac{g_m}{g_m + g_{ds} + G_S}$

$$v_o = v_i (1 + g_m/g_{ds}) = v_{in} \cdot \frac{g_m}{g_{ds}} \cdot \frac{g_m + g_{ds}}{g_m + g_{ds} + G_S}$$

$$\Rightarrow v_o/v_{in} = \underline{\underline{18.26}} \quad [15]$$

Intuitive approach

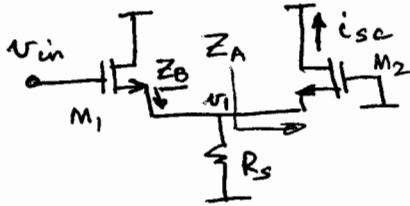We have already measured Z_{out} . Let's measure i_{sc} again.



Looking into M_2 from source, $Z_A = \frac{1}{g_m + g_{ds}}$

Looking at the load of M_1 at source, $Z_B = Z_A \parallel R_s$
 $= \frac{1}{g_m + g_{ds} + G_s}$

So the gain from v_{in} to the source of M_1 (source follower)

$$= \frac{Z_B \parallel r_{o1}}{Z_B \parallel r_{o1} + 1/g_{m1}} = \frac{\frac{1}{g_m + 2g_{ds} + G_s}}{\frac{1}{g_m + 2g_{ds} + G_s} + \frac{1}{g_{m1}}} = \frac{g_m}{2g_m + 2g_{ds} + G_s}$$

i.e. voltage $v_1 = v_{in} \cdot \frac{g_m}{2g_m + 2g_{ds} + G_s}$

Now $i_{sc} = + g_m v_1 + g_{ds} \cdot v_1 = v_{in} \cdot \frac{g_m (g_m + g_{ds})}{2g_m + 2g_{ds} + G_s}$

∞ $G_{min} = \frac{g_m (g_m + g_{ds})}{2g_m + 2g_{ds} + G_s} = 954.5 \mu S$

∞ $v_{out}/v_{in} = G_{min} \cdot \cancel{Z_{out}} \cdot Z_{out} = \underline{\underline{18.26}}$

General Comments:

For questions on small signal gain, Z_{out} etc, more than 50% marks has been awarded if you get just the circuit diagram correct. Beyond that, marks have been awarded according to work done.