


Designing Analog and RF Circuits for Ultra-low Supply Voltages

Peter Kinget



COLUMBIA UNIVERSITY
IN THE CITY OF NEW YORK

Nano CMOS : Supply Voltage

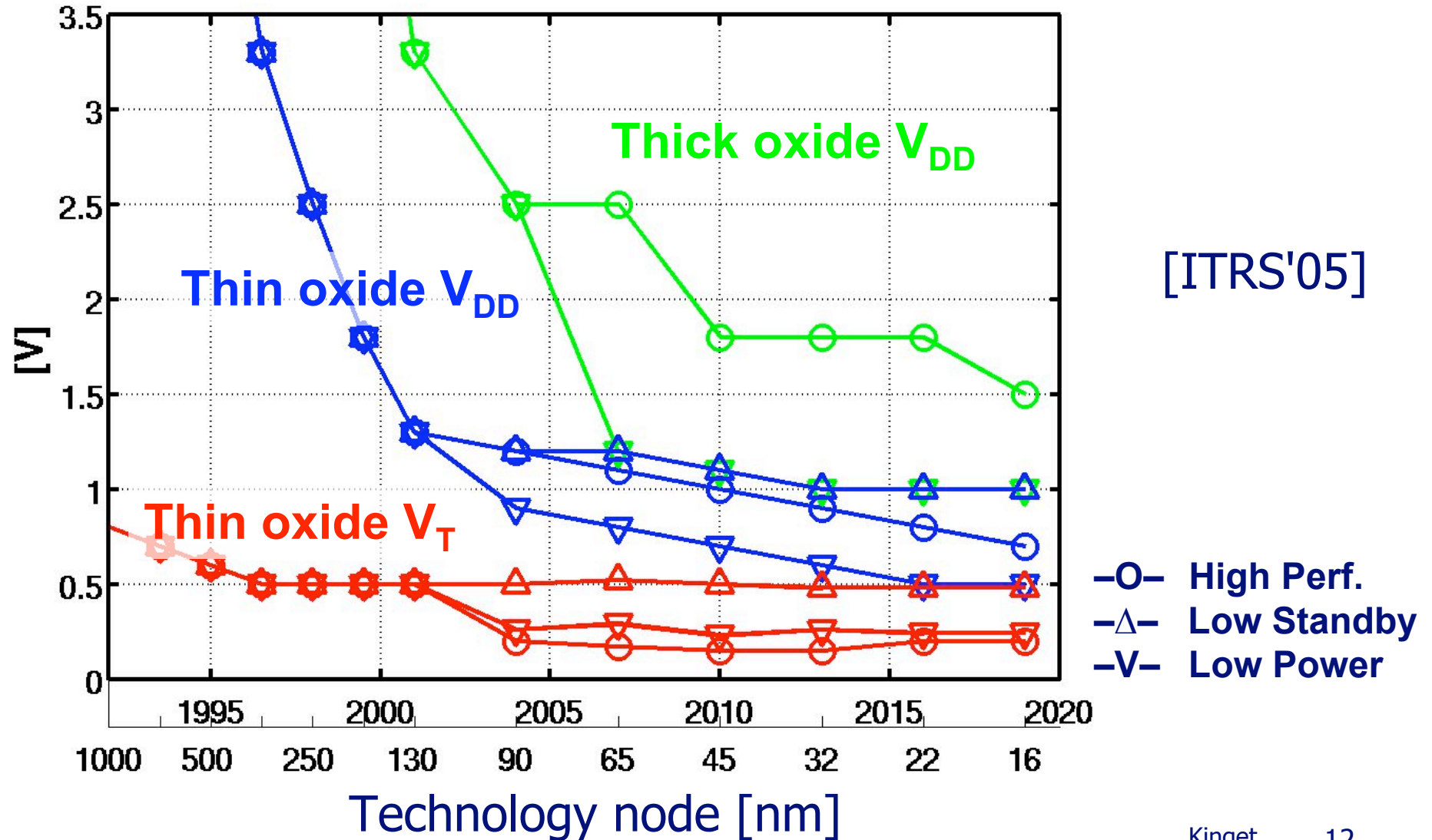



[ITRS'05]

- O- High Perf.
- △- Low Standby
- ▽- Low Power

Ultra-low Voltage Analog/RF


- What analog/RF is possible in core nanoscale digital?
- Scavenging applications
 - E.g., single solar cell V_{DD} 0.4-0.5V
- Ultra-low energy digital systems
 - Optimal DV_{DD} is 0.3-0.5V
 - Analog support functions for digital
- SOC designs
 - Analog/RF powered from on-chip LDO
 - AV_{DD} is 0.2V below DV_{DD}
- Interesting research...
 - Explore boundaries, develop design techniques

MOST Biasing: CS or VCCS

  


- Transconductor or Current Source
 $V_{DS} > 0.15 \text{ V}$ (for $V_{GS} - V_T \leq 0.2 \text{ V}$)
- Moderate to Strong Inversion
 $(V_{GS} - V_T) \approx 0.15 \text{ V}$ & $V_T = 0.15 \text{ V} \rightarrow V_{GS} = 0.3 \text{ V}$

Ultra-LV Challenges in OTAs


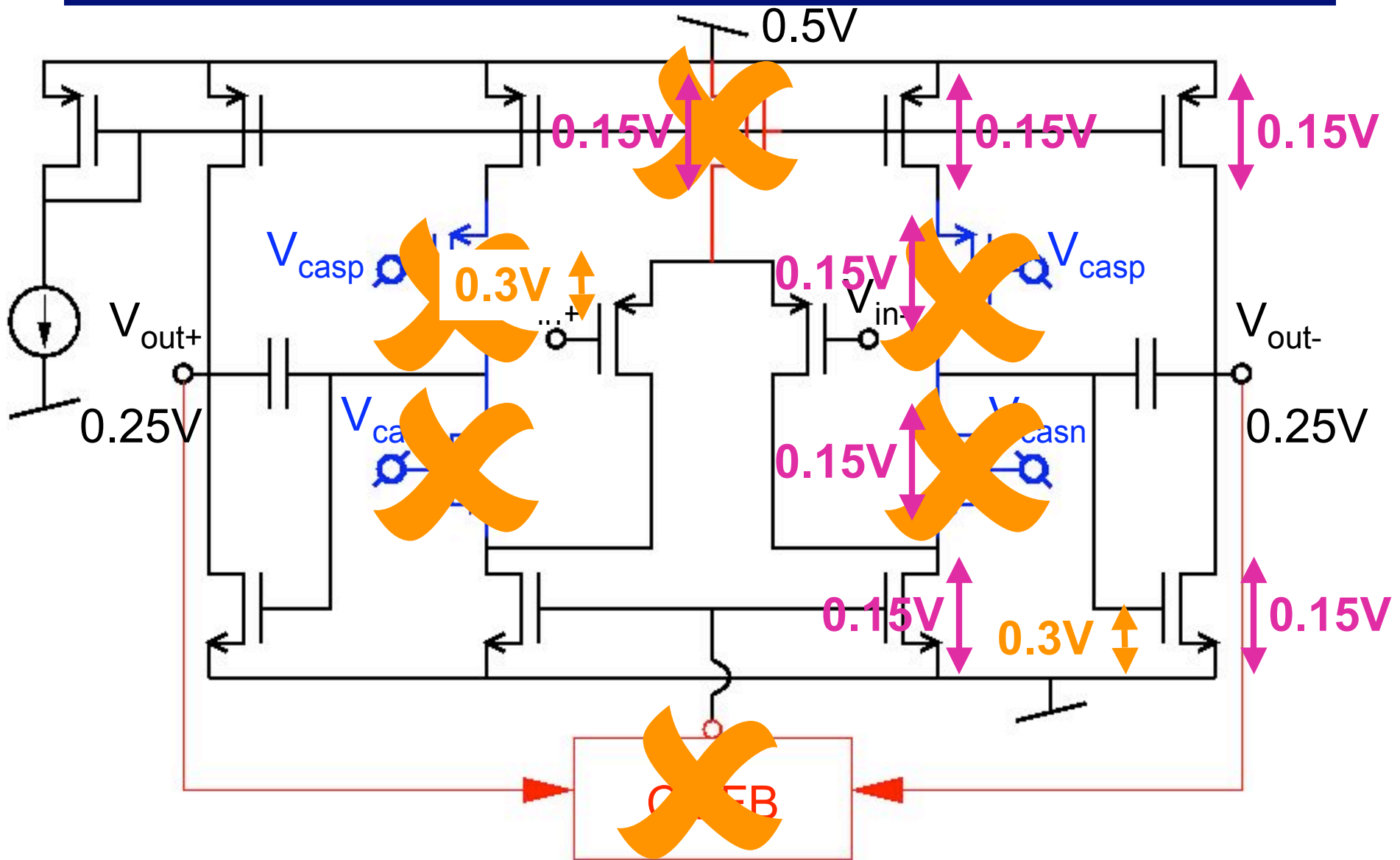


Device Level


- RSCE

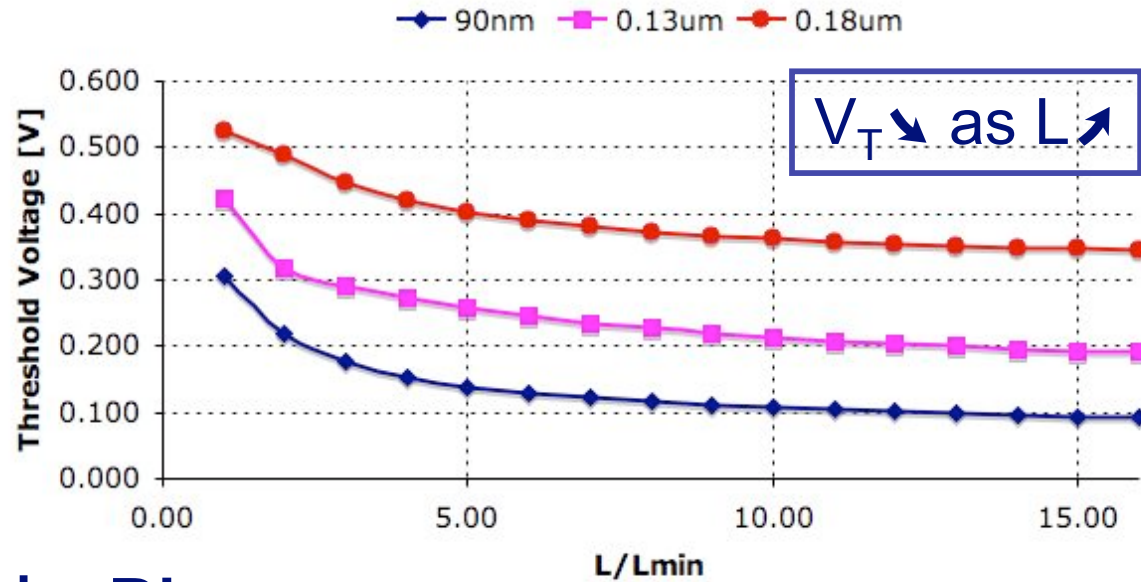


- Forward Body-Bias

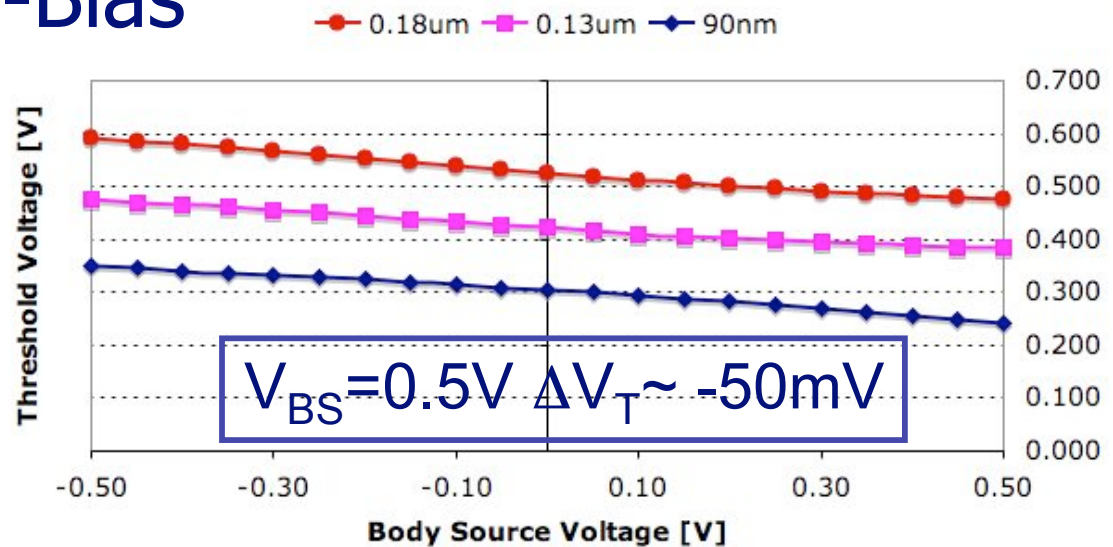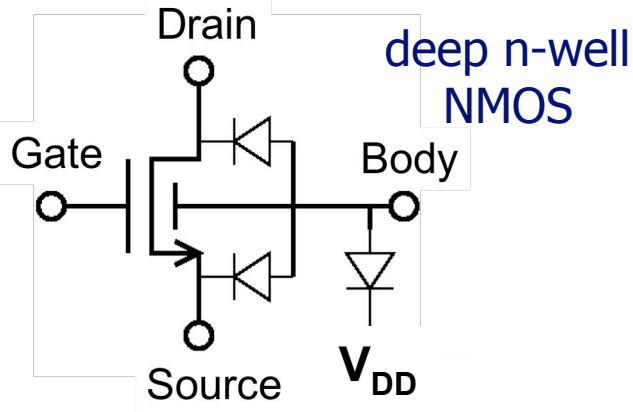


0.5 V Gate-input OTA stage

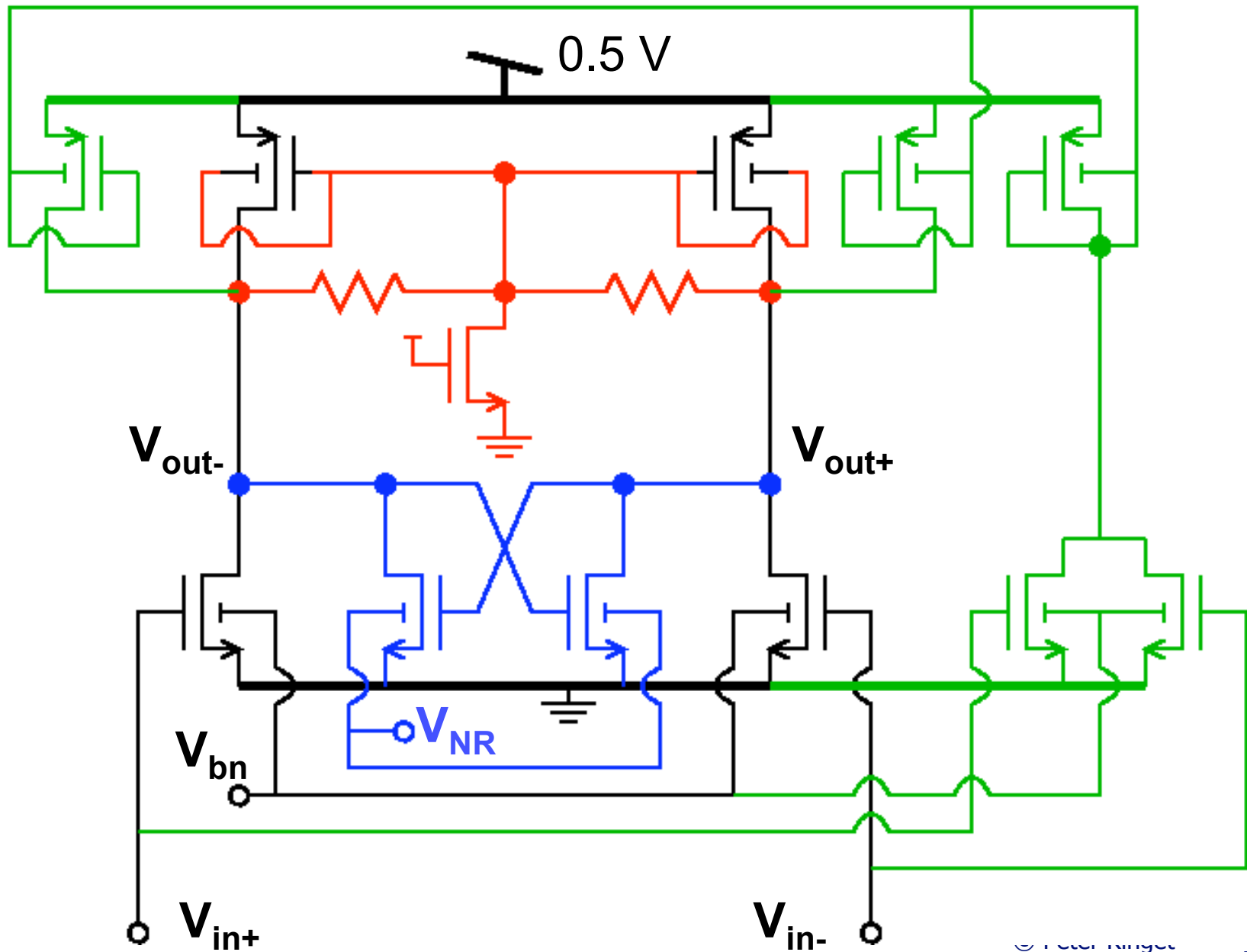


0.5 V OTA in 0.18 μ m CMOS

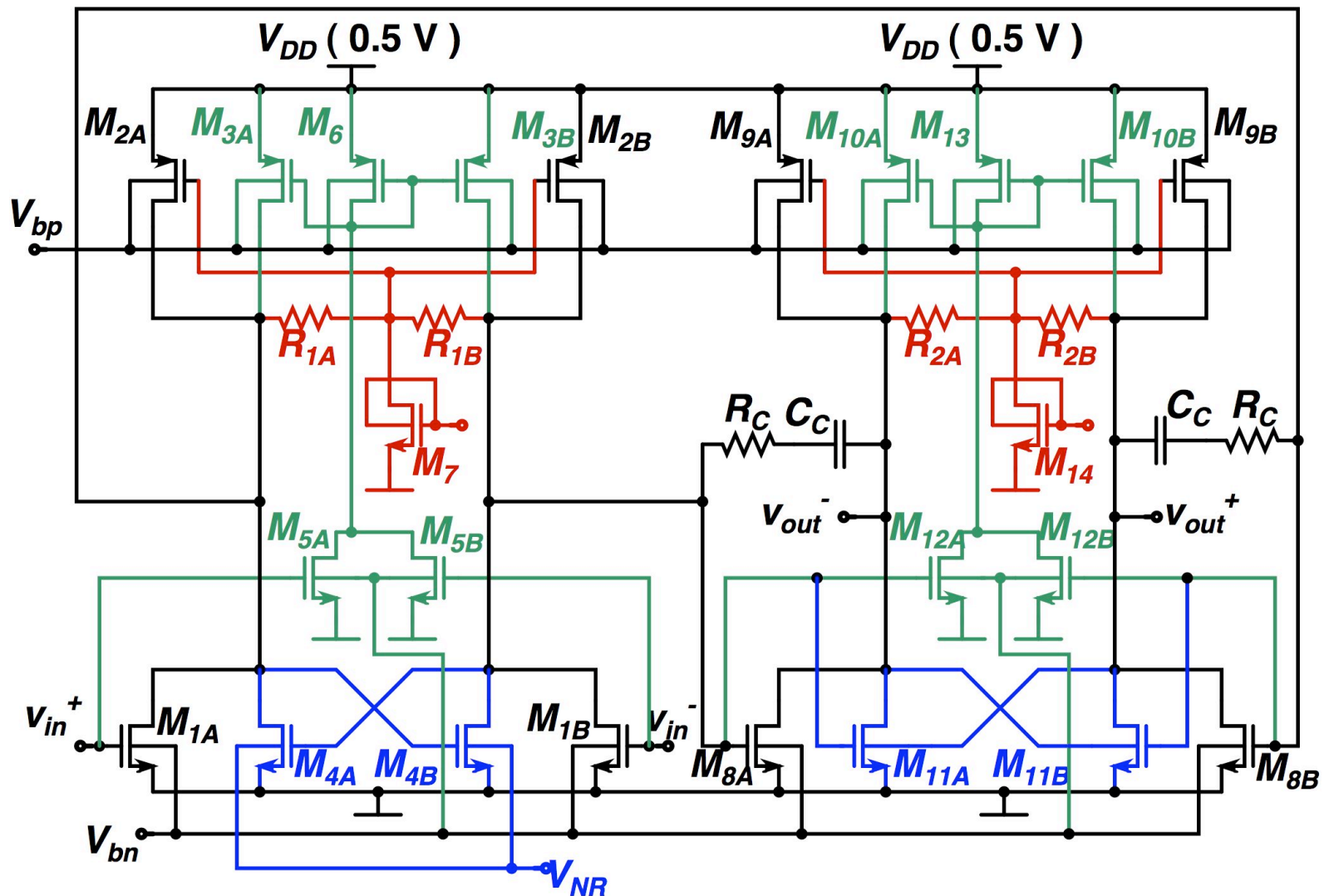


On-chip biasing circuits

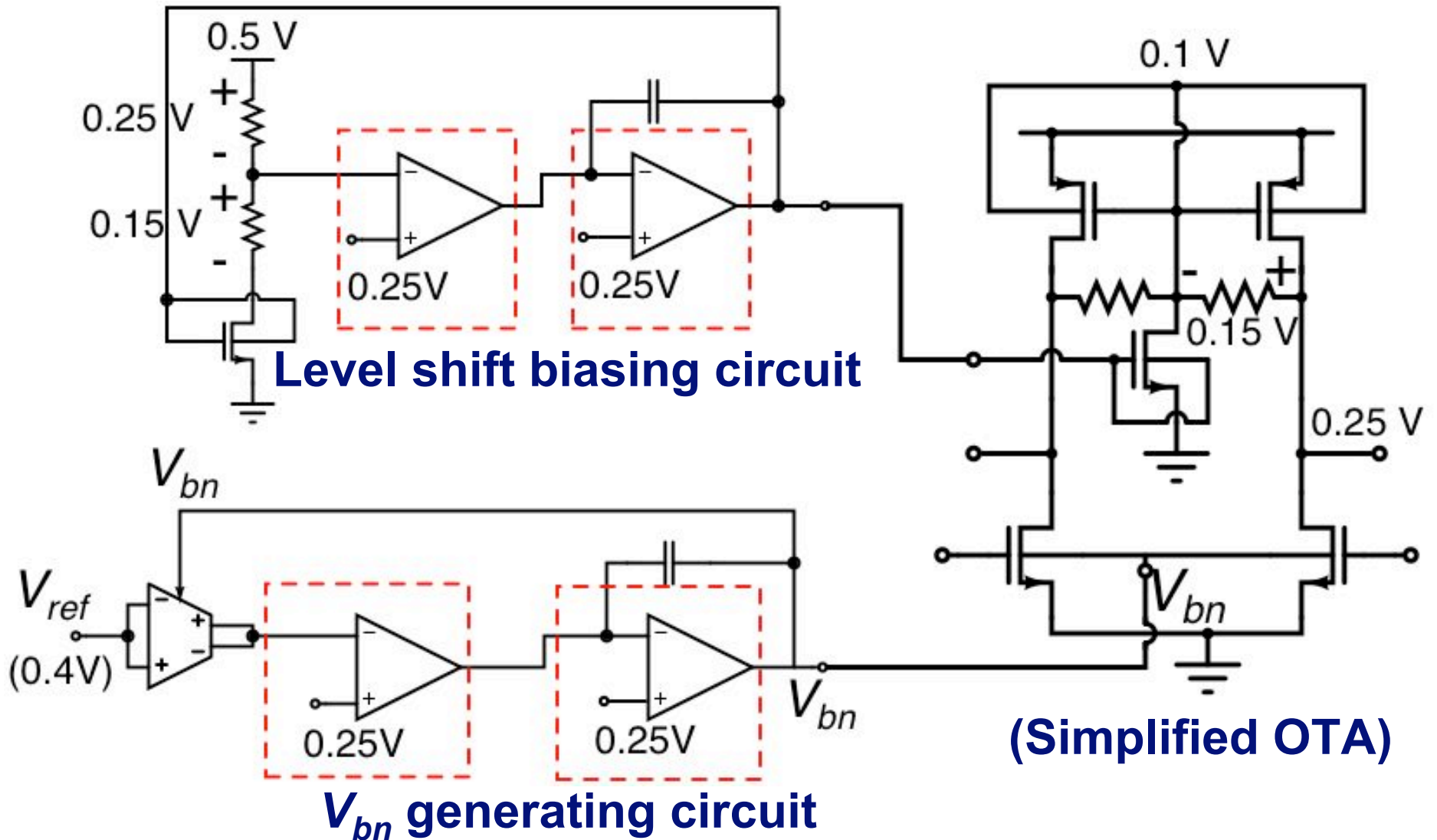


Error amplifier for biasing

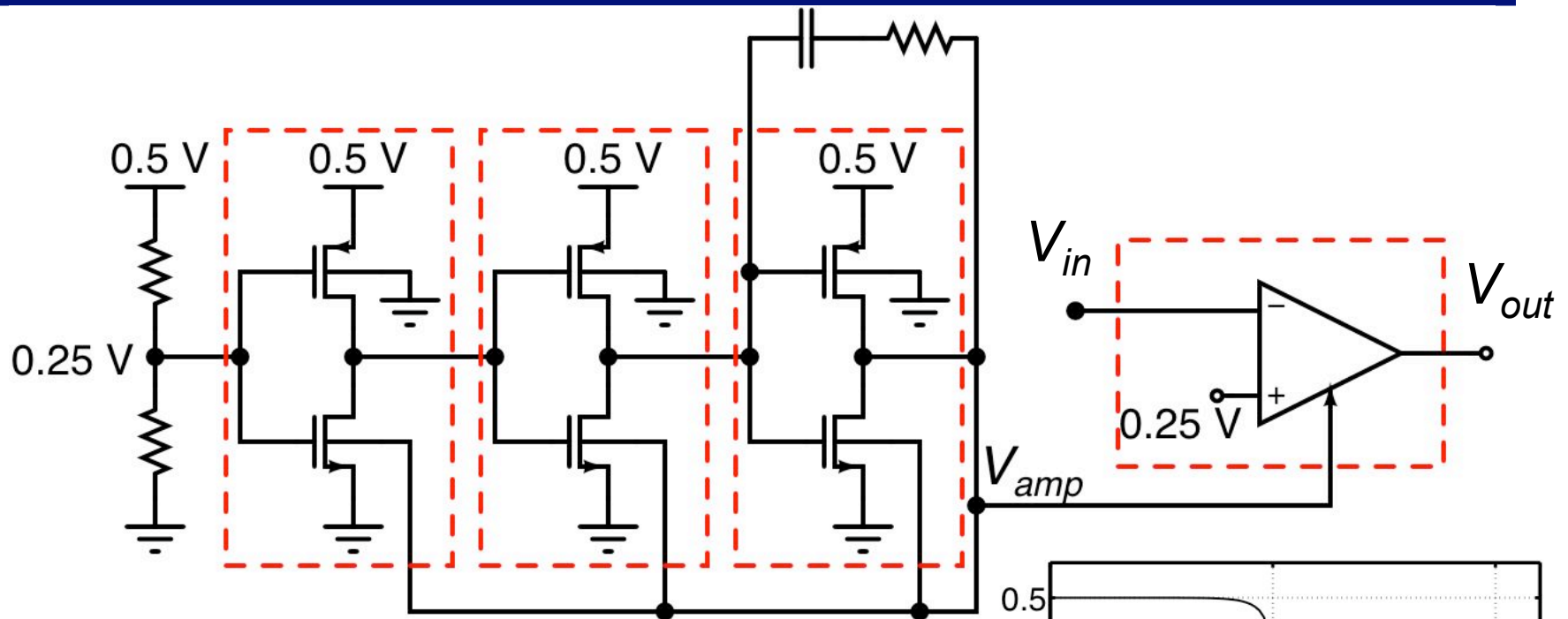

 
- 20 kHz GBW for 1 pF load
- 2 μ A current
- Controlled body voltage sets the amplifier threshold



 
OTA DC transfer characteristics and V_{NR} generation




V_{NR} generating circuit

 



Open loop performance (meas.)

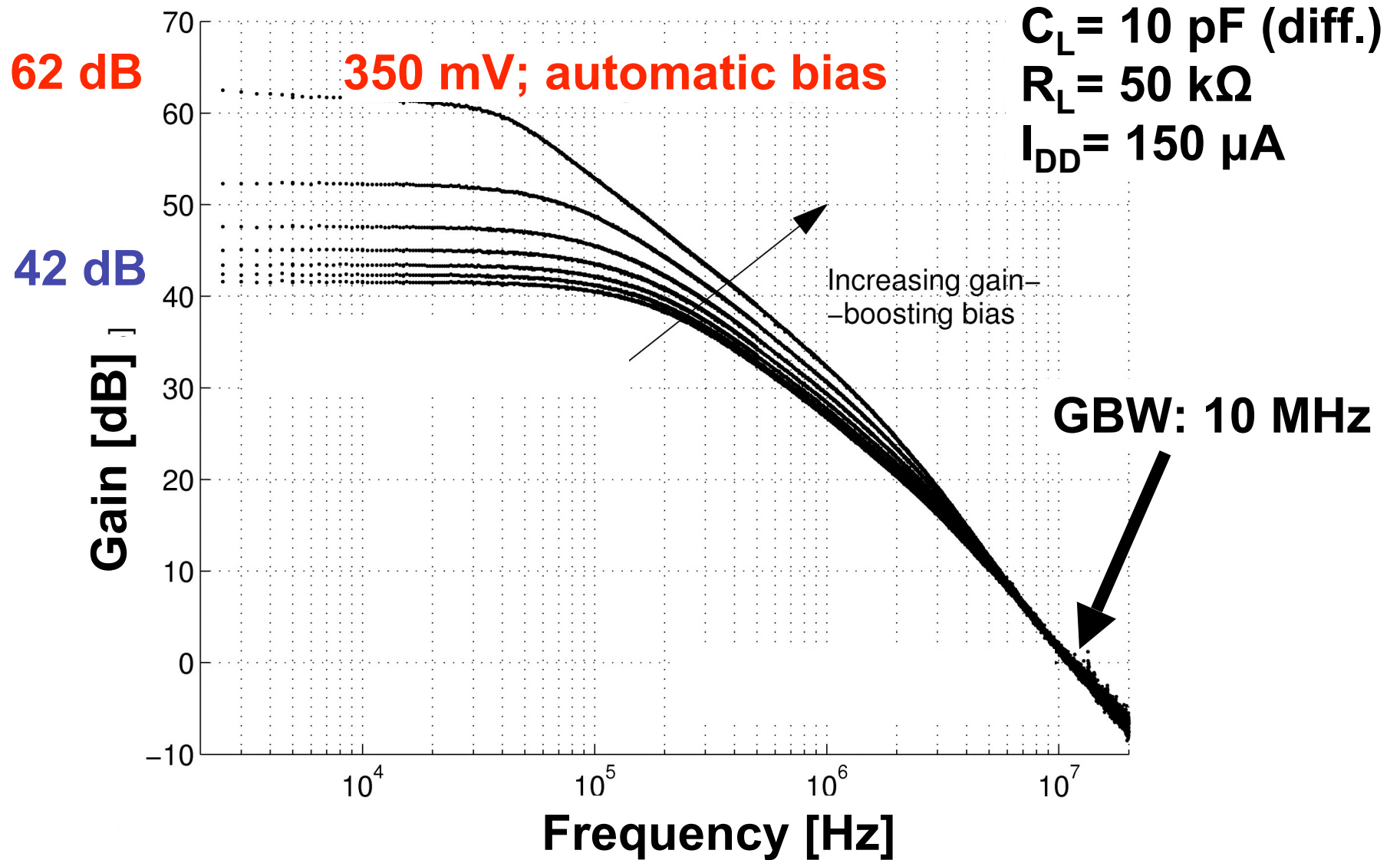

Low-voltage tunable integrator

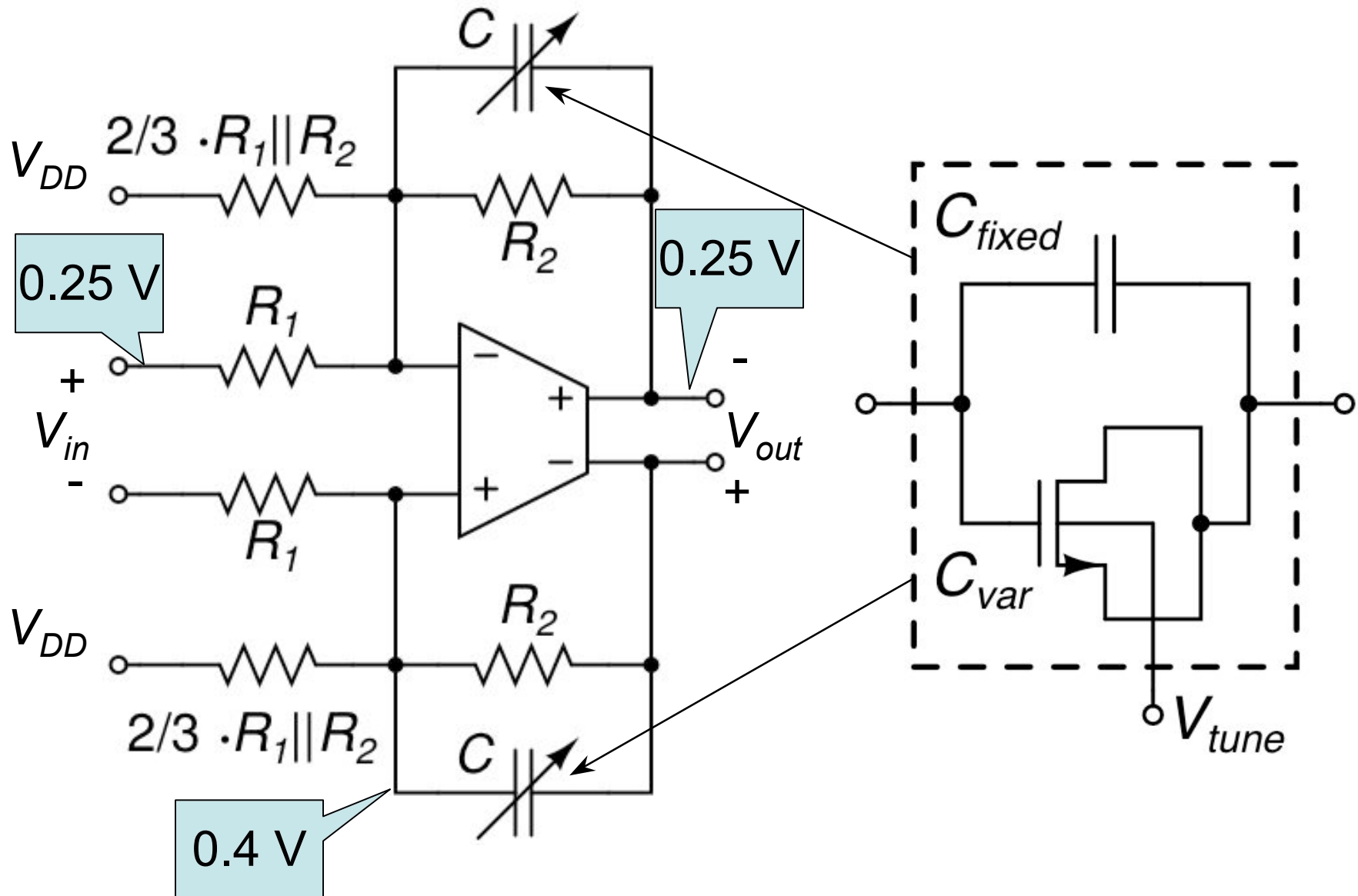

0.5 V Fully integrated 5th order LPF

 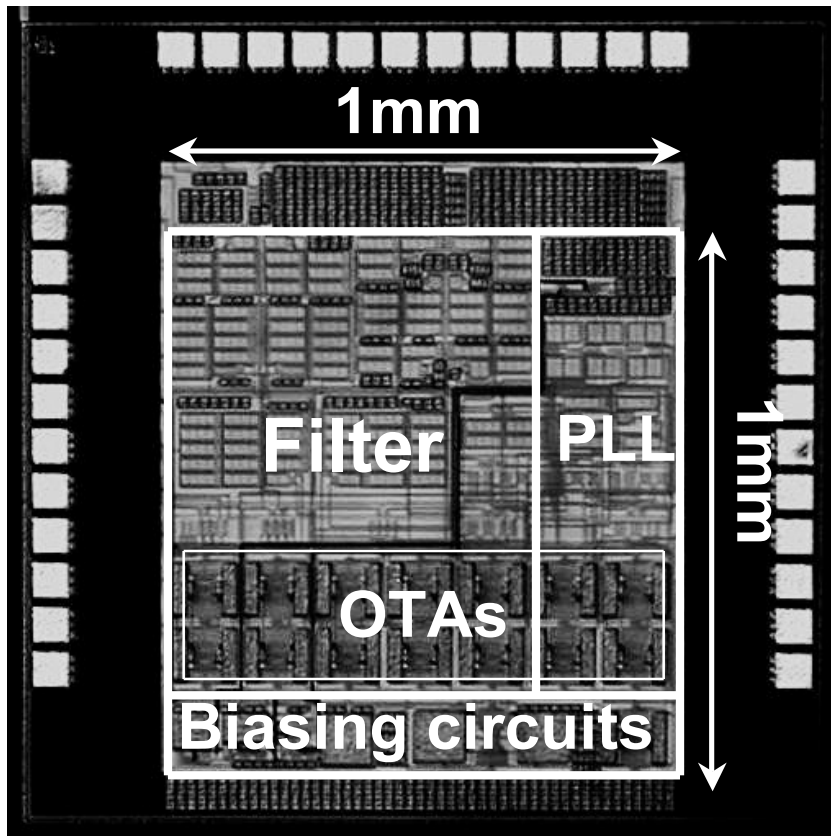

- Operation at 0.45 V to 0.6 V
- 1.1 mW power dissipation
- 57 dB dynamic range

[Chatterjee, ISSCC05,
JSSC05]


Performance summary at 27C

V_{DD} [V]	0.45	0.50	0.55	0.60	
-3 dB cut-off frequency [kHz]	135.0	135.0	135.0	135.0	
Total current [mA]	1.5	2.2	3.3	4.3	
Noise [μ V rms]	87	74	68	65	
Input [mV rms] (100kHz / 1% THD)	50	50	50	50	
In-band IIP ₃ [dBV]	-5	-3	-3	-3	
Out-of-band IIP ₃ [dBV]	3	5	3	5	
Dynamic range [dB]	55	57	57	58	
Tuning range [kHz]	$V_{tune} = V_{DD}$	96.5	88.0	84.5	69.0
	$V_{tune} = 0.0$ V	153.0	154.5	148.0	150.5
VCO feed-thru @280kHz [μ V rms]	104	85	72	72	

- Measured CMRR (10 kHz common mode tone): 65 dB
- Measured PSRR (10 kHz tone on power supply): 43 dB


Functionality tested from 5C to 85C at 0.5 V

0.5V 1Msps 60dB T/H amplifier

 


- True low voltage
- No clk boosting
- [Chatterjee, VLSI 06, JSSC07]

- 0.25 μm CMOS
- $|V_t| = 0.6\text{V}$
- 60dB SNDR
- 1Msps
- 0.6mA at 0.5V

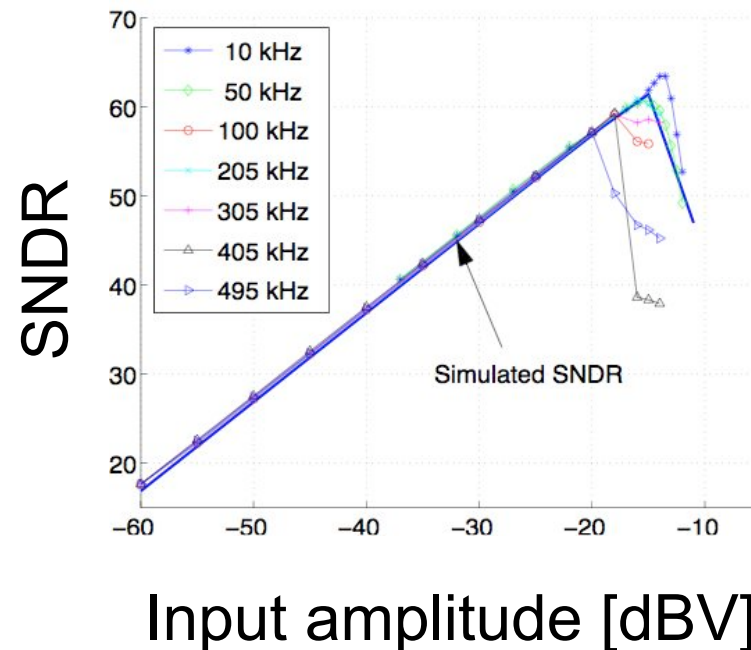


0.5V Differential Track and Hold

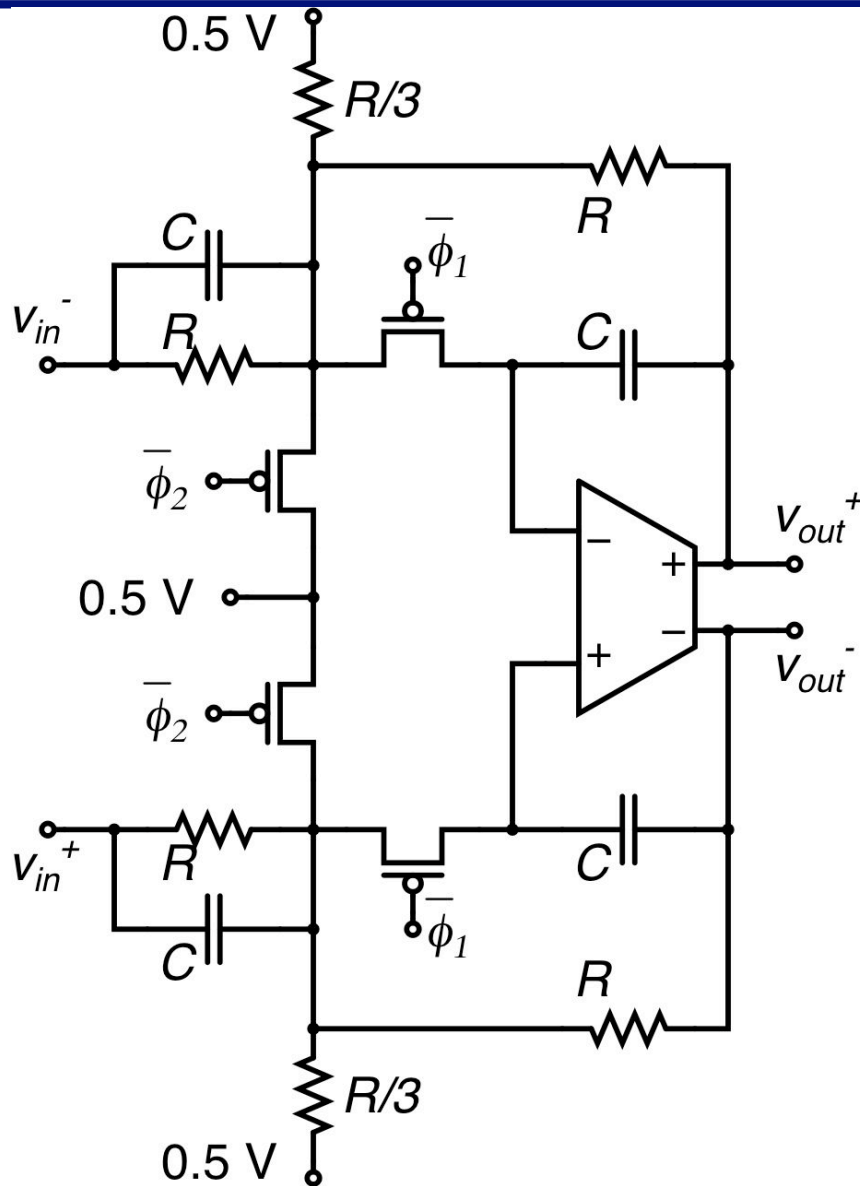


- Gate-input OTA used.
- Track phase during ϕ_1 , hold phase during ϕ_2 .
- During track phase, pole and zero cancel out to enable fast response.
- pMOS switches have V_T of about 0.5V.

Track mode operation

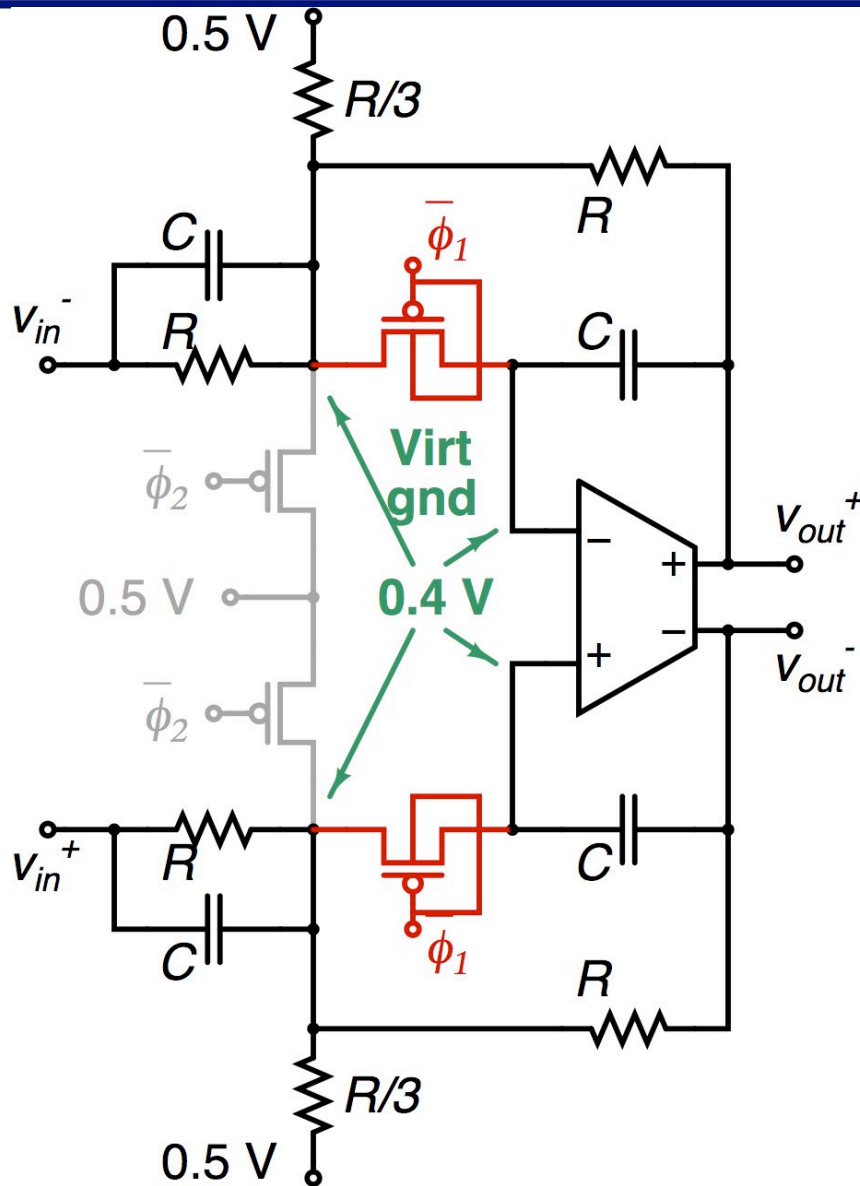


- Resistors to 0.5V maintain required OTA input CM voltage of 0.4V.
- To enable better switching, both gate and body of the switch are used.
- No voltage swing on either side of the switches.

Hold mode operation

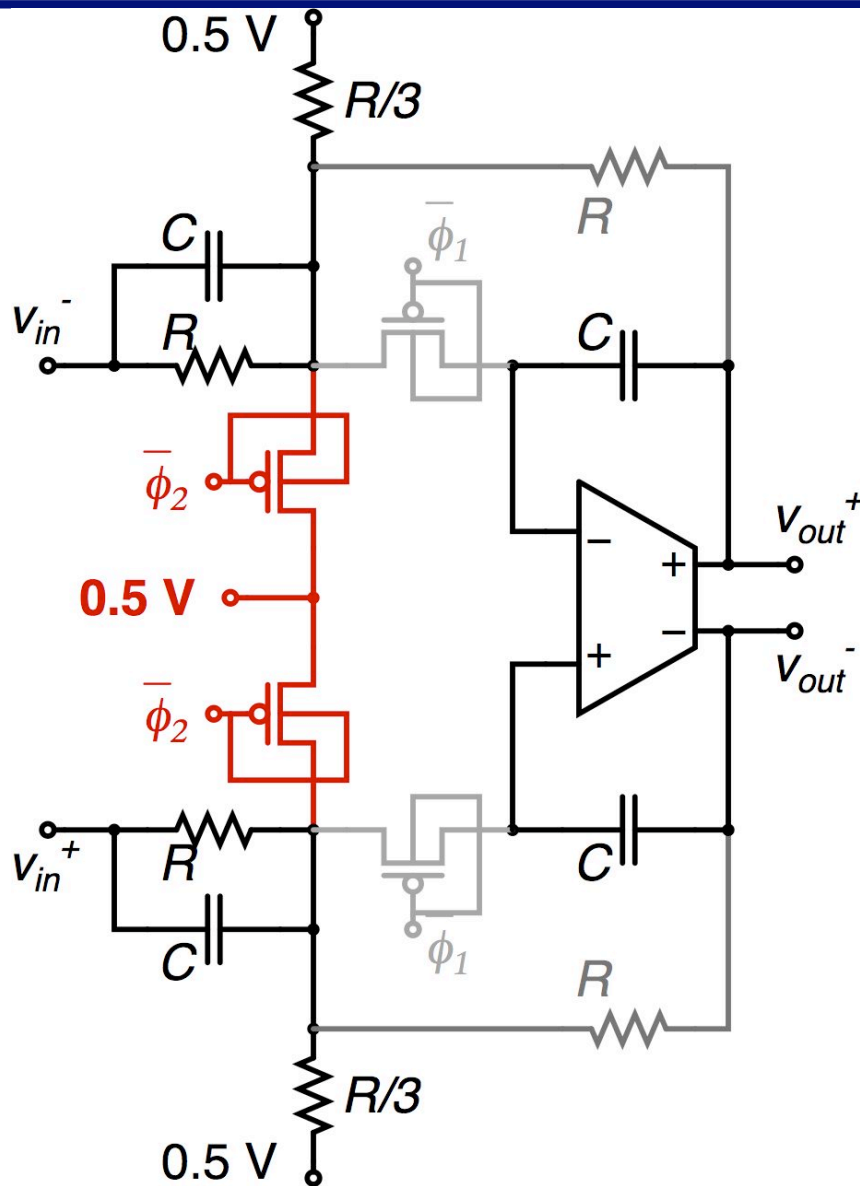

- Gate and body of the switch used for better switching.
- No signal swing on both sides of the switches.
- OTA input voltages held constant.


Measured SNDR

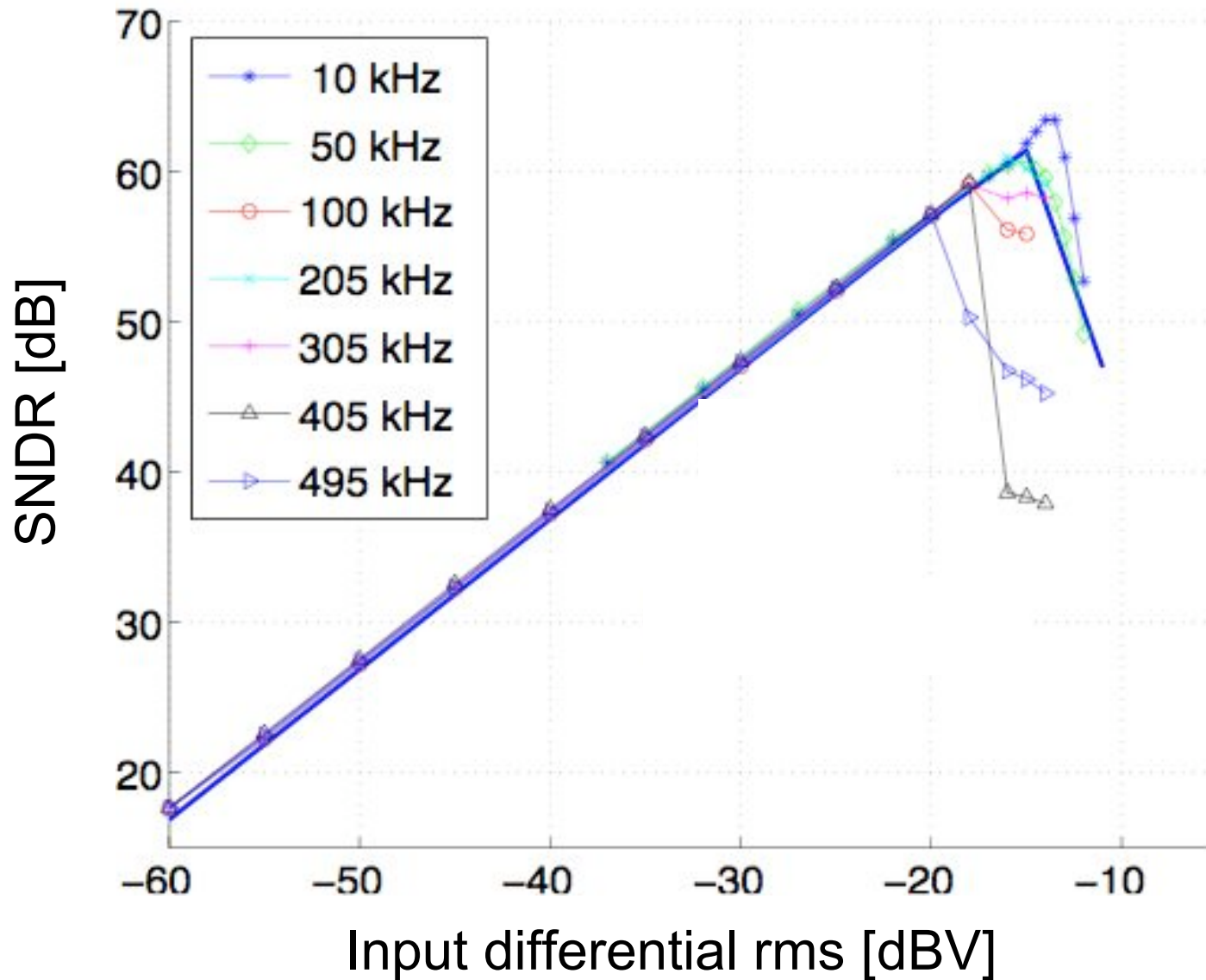

Measured performance

Power supply	0.5V
Current consumption	600 μ A
Sampling rate	1Msps
Diff. input refd. integrated noise	188 μ V _{RMS}
Peak SNDR $f_{IN}=50\text{kHz}$; $V_{in,diff}=178\text{mV}_{RMS}$	60dB
Peak SNDR $f_{IN}=495\text{kHz}$; $V_{in,diff}=100\text{mV}_{RMS}$	57dB
Hold mode droop rate on diff. output	7.6 μ V/ μ V
Pedestal on diff. output	0.8mV
Track mode bandwidth	3.9MHz

 0.5 V 74 dB SNDR 25kHz $\Sigma\Delta$ Modulator




- 0.18 μm CMOS
- MIM caps
- Triple-well devices
- High-res resistors

- Body-input, gate-clocked logic
- Return-to-open feedback

- [Pun, Chatterjee, Kinget, ISSCC 06]

3rd order CT $\Sigma\Delta$ Modulator


Using Active RC integrators

 

3rd order CT $\Sigma\Delta$ Modulator

Using Active RC integrators


Using Body-Input OTAs (2stages)

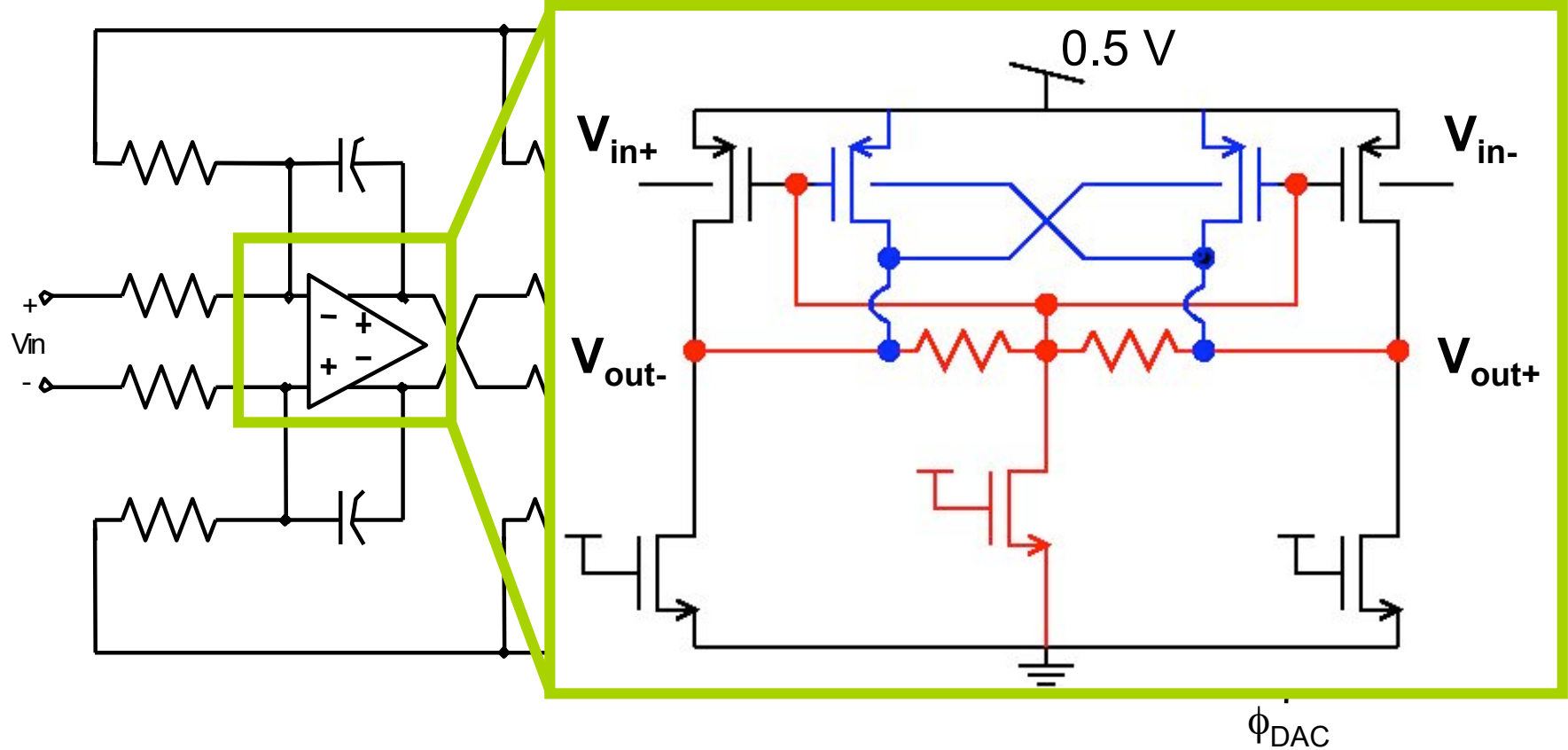

3rd order CT $\Sigma\Delta$ Modulator


Using Active RC integrators

Gate-clocked Body-input Comparator


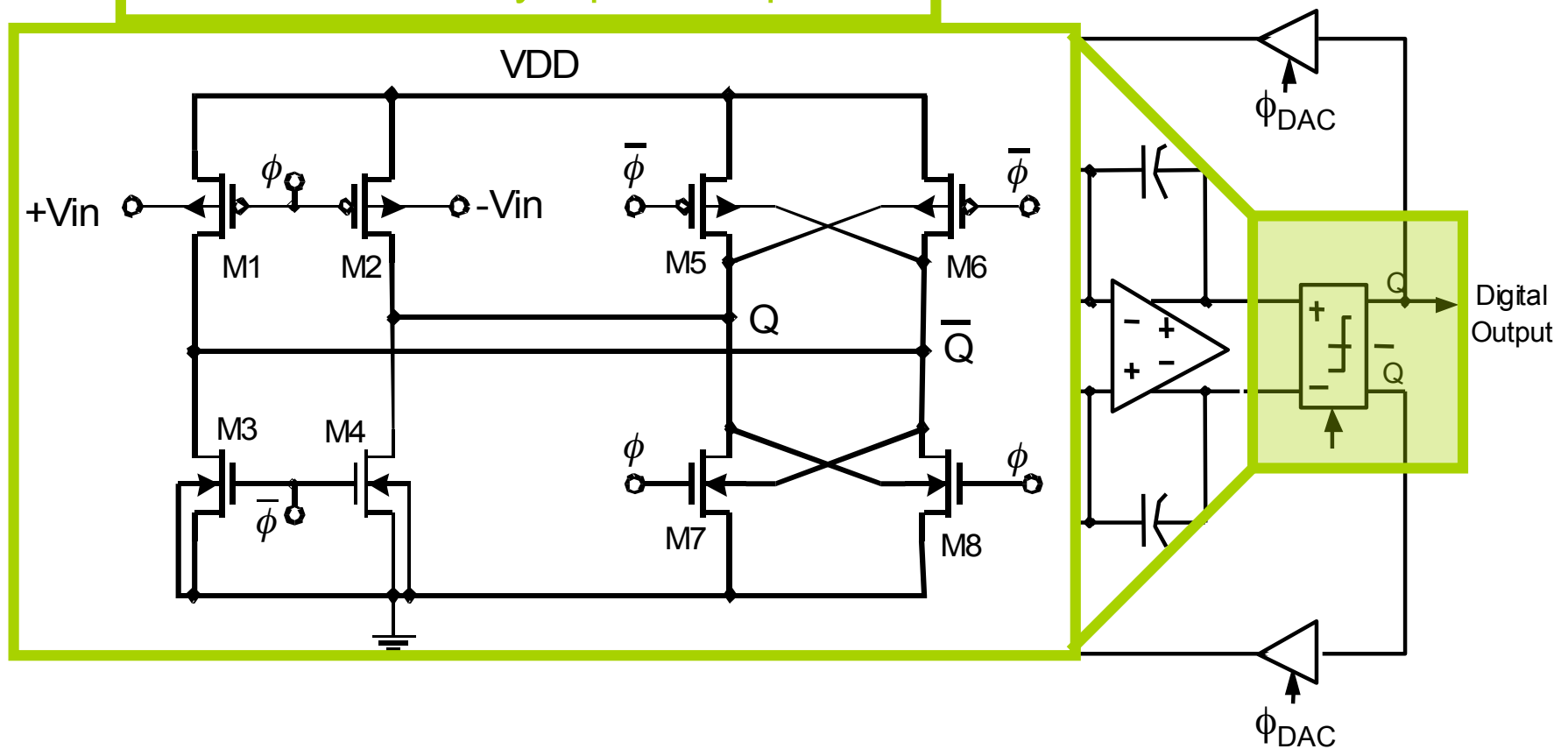


3rd order CT $\Sigma\Delta$ Modulator


Using Active RC integrators

 

RZ Challenge: Switches at $V_{DD}/2$


 
 


Switch Conductance

 




Solution: Return-to-Open

When RZ:
(Q=1)

  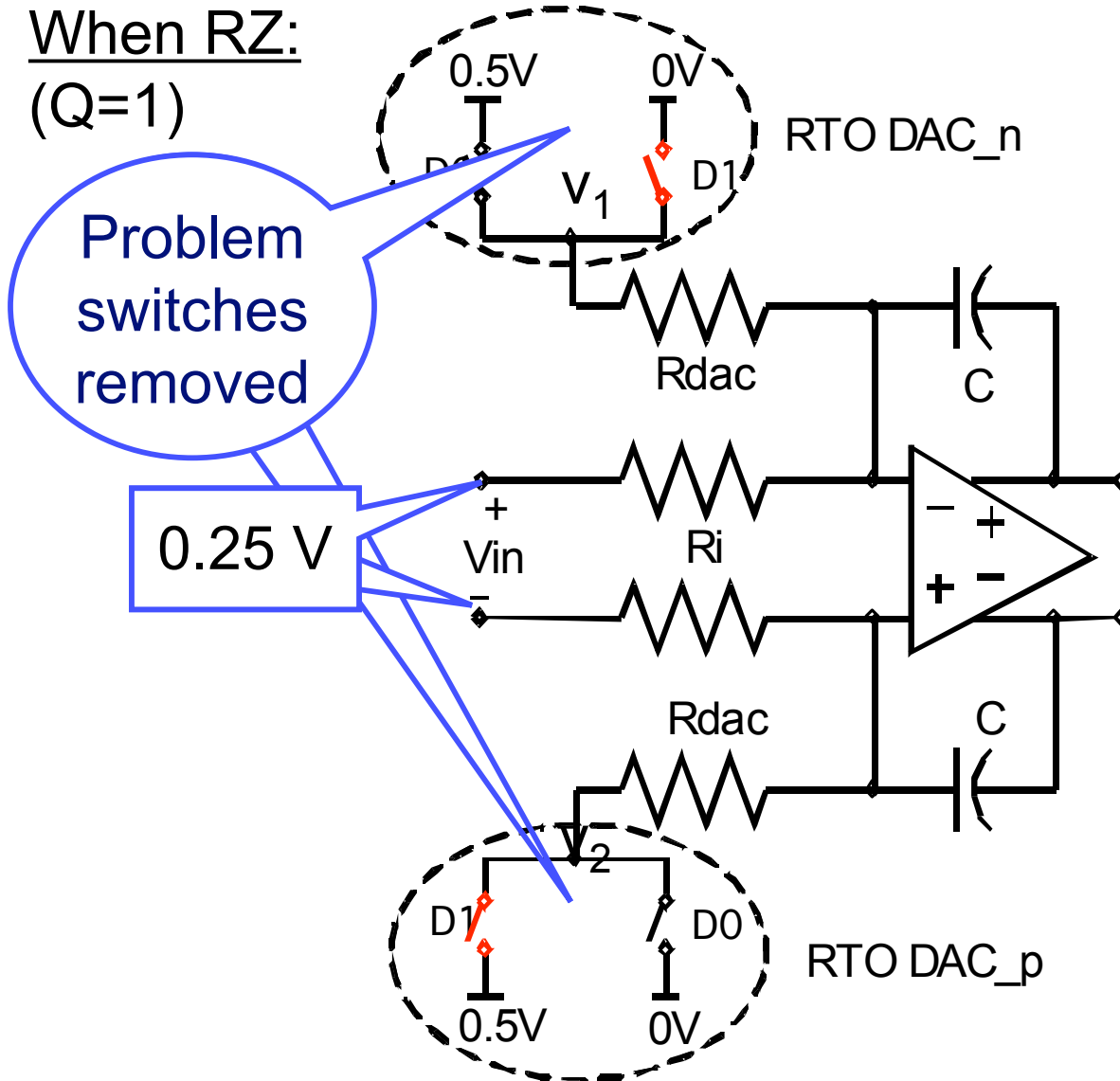


Solution: Return-to-Open


When RZ:
(Q=1)

 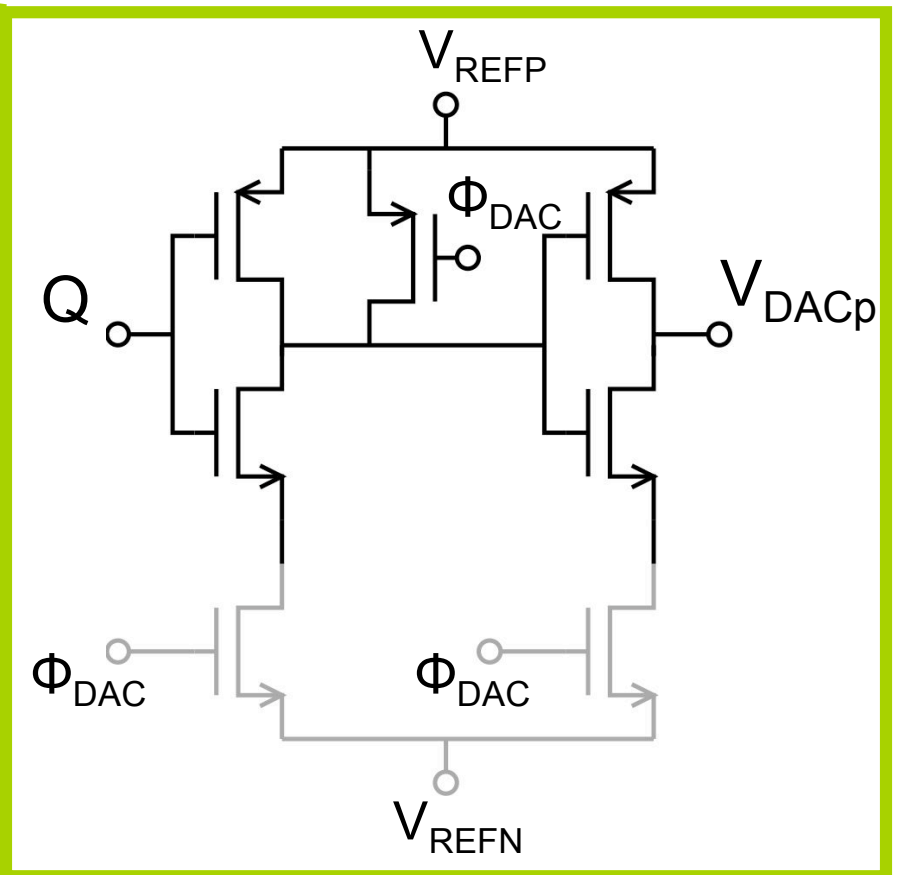 

Problem switches removed

 

Return-to-open CT SDM

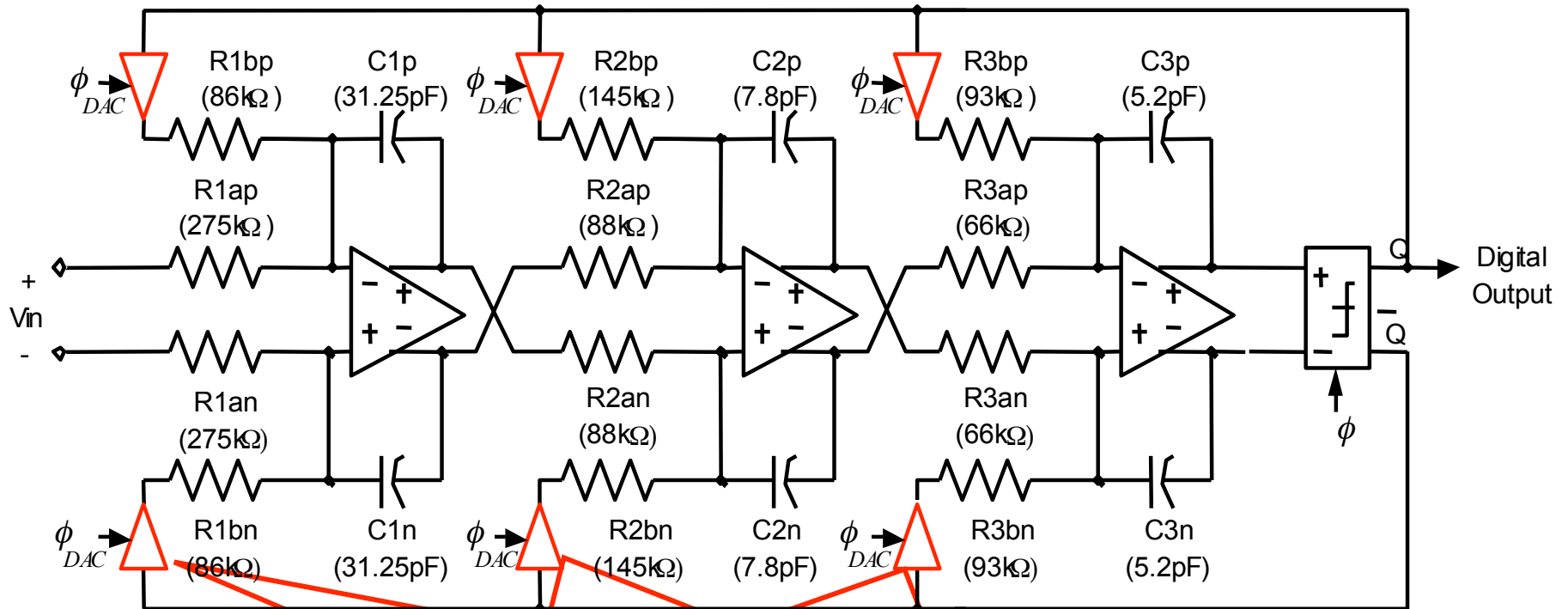

Split Return-to-open DAC


Only switches to VDD or VSS

BW = 25kHz, $f_s = 3.2\text{MHz}$,
 $V_{in,max} = 1\text{Vppdiff}$.


Performance Summary at 25°C

Modulator type	1-bit, 3rd order, continuous-time		
Signal bandwidth	25 kHz		
Sampling frequency / OSR	3.2 MHz / 64		
Input range	1 V _{ppdiff.}		
Supply Voltage	0.45V	0.5V	0.8V
SNDR @ V _{in} = 1V _{ppdiff.}	71 dB	74 dB	74 dB
SNR @ V _{in} = 1V _{ppdiff.}	76 dB	76 dB	74 dB
Power consumption (total)		370 μW	
Sigma Delta Modulator		300 μW	
Output buffers		70 μW	
Active die area	0.6 mm ²		
Technology	0.18 μm CMOS (standard V _T , triple-well, MIM, and HiRes Poly)		


Recent Work in 90nm CMOS

 

 0.65/0.5V 2.4-2.6GHz
Fractional N
Freq. Synthesizer




 0.5V 2.4GHz Sliding-IF
Receiver + I/Q Baseband





0.5V 10Msps 8bit
Pipelined ADC

 0.65V/0.5V 2.4-2.6GHz Fractional-N Synthesizer



- Swings on all VCO nodes are kept within the supply rails for reliability.
- Forward body bias to enhance the divider speed.
- Fractional-N DSM dithering shifted to later divider stages to prevent noise injection into forward biased body.
- Staggered clock to prevent jittering caused by simultaneous switching.
- 90nm CMOS
- [S. Yu & P. Kinget, ISSC07]


Performance Summary

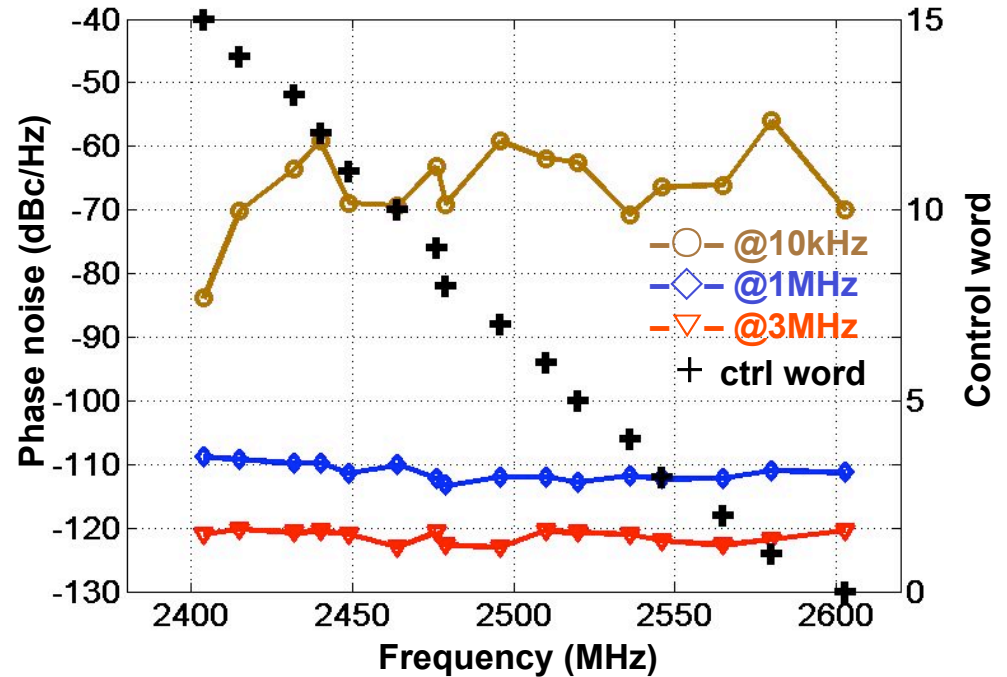 

- AVDD 0.5V - 2.5mW
- DVDD 0.65V - 3.5mW
- 0.14mm² - 90nm CMOS
- RVT devices

 
- 2.4-2.6GHz
- Phase noise:
-120dBc/Hz @ 3MHz
- Spurs: -52dBc

A 0.5V 8bit 10MSPS Pipelined ADC in 90nm CMOS




- No internal voltage or clock boosting
- Regular devices
- Cascaded sampling technique to reduce the channel leakage of the switches
- 1.5bit/stage (remark: stages identical, stages scaling not exploited)
- Front-end S/H amplifier eliminated by with an S/H for the sub-ADC.
- 0.5V OTAs with local CMFB
- 90nm CMOS
- [J. Shen & P. Kinget, VLSI07]

A 0.5V 2.4GHz Receiver

 


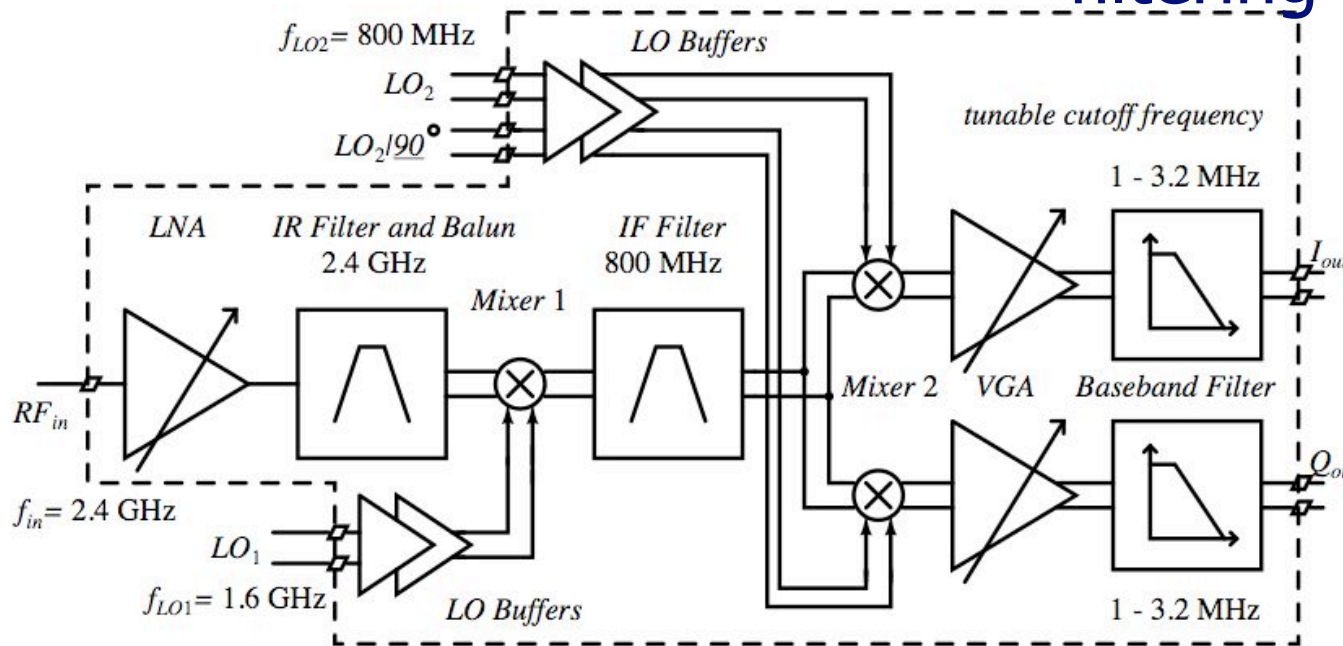- ISM band applications
- Sliding IF topology
- LNA, Mixers, VGA + on chip RF, IF & BB filtering



[Stanic, Balankutty, Kinget, Tsvividis, RFIC07]


0.5V Analog Roadmap

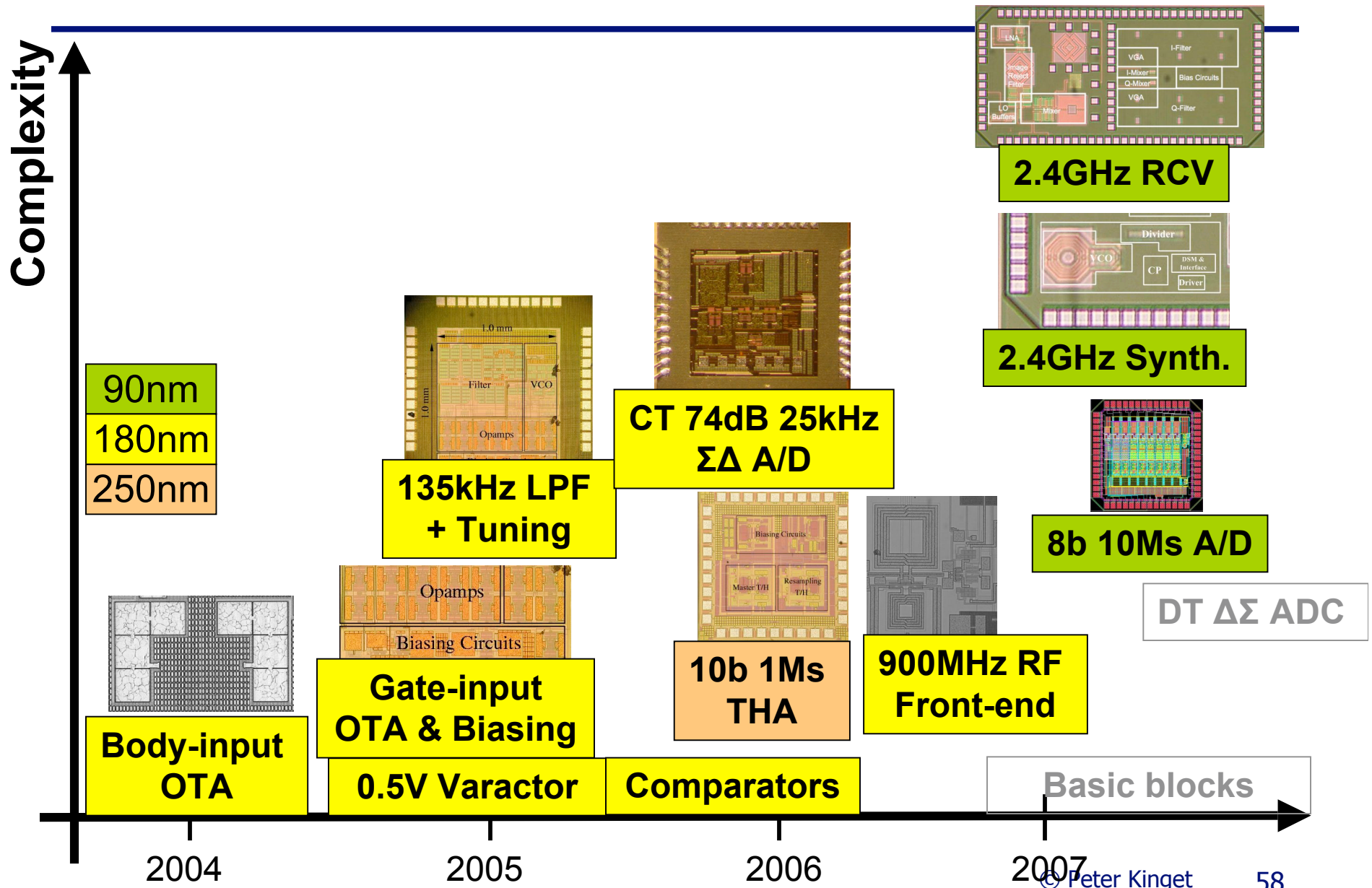

Where do we go from here...

- Other nanoscale challenges:
 - Gate & subthreshold (OFF) leakage,
 - Smaller g_m/g_o ,
 - Reduced body effect.
- Opportunities
 - Device speed significantly improves:
 - Scale device operating points for larger (g_m/I_D) ,
 - FinFETs, dual gate devices,
 - Calibrate using abundant digital gates.
- But, some fundamental limitations are against us...

Power Dissipation Limits

 

- Noise limited circuits [Vittoz90]:

$$SNR = \frac{V_{RMS}}{\sqrt{v_{n,RMS}^2}} \quad \overline{v_{n,RMS}^2} = \frac{kT}{C} \quad I_{DC} = 2fC\sqrt{2}V_{RMS}$$

$$P \geq 8 kT f SNR^2$$

ideal class B

- Mismatch limited circuits [Kinget96]:



$$Acc = \frac{V_{RMS}}{3\sigma(V_{os})} \quad \sigma^2(V_{os}) = \frac{C_{ox}A_{VT}^2}{C} \quad I_{DC} = 2fC\sqrt{2}V_{RMS}$$

$$P \geq 24 C_{ox} A_{VT}^2 f Acc^2$$

Low Voltage Power Penalty

- Finite V_{DSsat} :

 
 
$$V_{DD} = 2\sqrt{2} V_{RMS} + 2V_{DSsat}$$



$$\text{Penalty factor} = 1 + \frac{2V_{DSsat}}{(V_{DD} - 2V_{DSsat})}$$

LV Challenge: Interfaces

0.5 - 1.0V

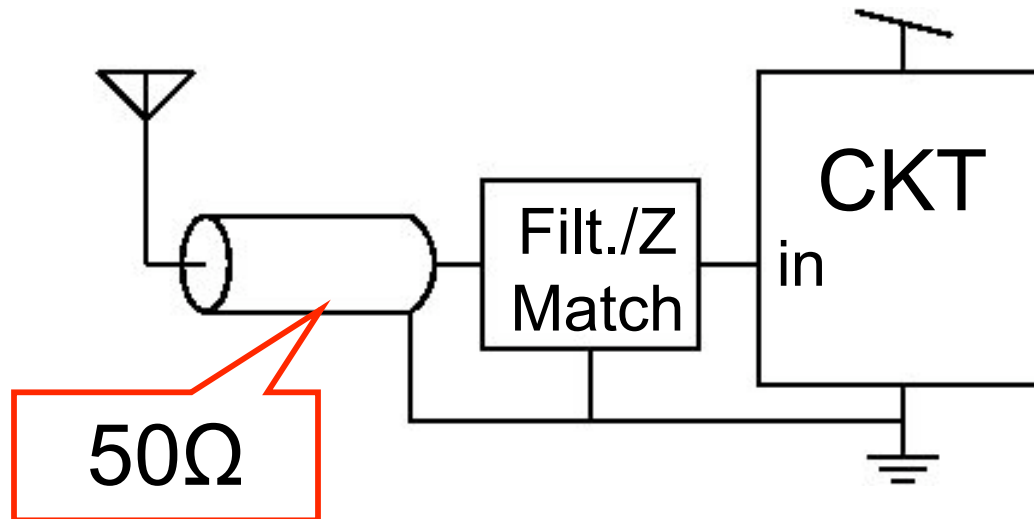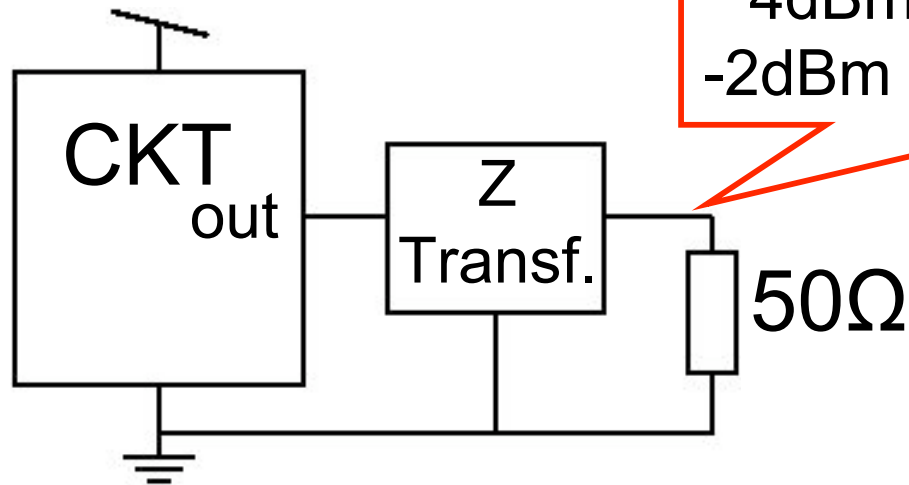

Ultra Low Voltage Analog Design Techniques

- Device Level:
 - Use body terminal for bias control or signal,
 - Use RSCE, optimize L to reduce V_T .
- Building Block Level:
 - Eliminate transistor stacks,
 - Use LCMFB, CMFF & Neg. G.
- Functional Level:
 - Revise signaling & architecture,
 - New tuning & biasing strategies.
- Demonstrated in 0.5V analog & RF building blocks & systems:
 - filters, THA, ADCs, RF front-ends, freq. synthesizers,
 - in 0.18um CMOS ($|V_T|=V_{DD}$) & 90nm CMOS.

Selection of Recent Publications

0.5V Analog/RF Integrated Circuits:

- S. Chatterjee, K.P. Pun, N. Stanic, Y. Tsvividis and P. Kinget, "Analog Circuit Design Techniques at 0.5V", Springer, in press, 2007.
- J. Shen, and P. Kinget, "A 0.5V 8bit 10MSPs Pipelined ADC in 90nm CMOS," IEEE Symposium on VLSI circuits, accepted, June 2007.
- N. Stanic, A. Balankutty, P. Kinget, and Y. Tsvividis, "A 0.5 V Receiver in 90 nm CMOS for 2.4GHz Applications," IEEE Radio Frequency Integrated Circuits Conference (RFIC), accepted, June 2007.
- S.A. Yu and P. Kinget, "A 0.65V 2.5GHz Fractional-N Frequency Synthesizer in 90nm CMOS" in Digest of Technical Papers IEEE International Solid-State Circuits Conference (ISSCC), Feb. 2007.
- S. Chatterjee, and P. Kinget, "A 0.5-V 1-MSPs Track-and-Hold Circuit with 60-dB SNDR," IEEE Journal of Solid-State Circuits, vol. 42, no. 4, pp. 722-729, Apr. 2007.
- K.P. Pun, S. Chatterjee, and P. Kinget, "A 0.5-V 74-dB SNDR 25-kHz Continuous-Time Delta-Sigma Modulator with a Return-to-Open DAC," IEEE Journal of Solid-State Circuits, Vol. 42, no 3, pp. 496-507, March 2007.
- N. Stanic, P. Kinget and Y. Tsvividis, "A 0.5 V 900 MHz Receiver Front End", IEEE Symposium on VLSI Circuits, June 2006.
- S. Chatterjee, Y. Tsvividis and P. Kinget, "0.5 V Analog Circuit Techniques and Their Application in OTA and Filter Design," IEEE Journal of Solid-State Circuits, vol. 40, no 12, pp. 2373 - 2387, Dec. 2005.

RF Integrated Oscillators:

- B. Soltanian, H. Ainspan, W. Rhee, D. Friedman and P. Kinget, "An Ultra Compact Differentially Tuned 6 GHz CMOS LC VCO with Dynamic Common Mode Feedback", IEEE Journal of Solid-State Circuits, in press, 2007.
- B. Soltanian, and P. Kinget, "A Low Phase Noise Quadrature LC VCO Using Capacitive Common-Source Coupling", European Solid-State Circuits Conference, pp. 436-439, Sept. 2006
- F. Zhang and P. Kinget, "Design of Components and Circuits Underneath Integrated Inductors" IEEE Journal of Solid-State Circuits, vol. 41, no. 10, pp. 2265-2271, Oct. 2006.
- B. Soltanian and P. Kinget, "AM-FM Conversion by the Active Devices in MOS LC-VCOs and its Effect on the Optimal Amplitude", IEEE RFIC Symposium, June 2006.
- B. Soltanian and P. Kinget, "Tail Current-Shaping to Improve Phase Noise in LC Voltage Controlled Oscillators " IEEE Journal of Solid-State Circuits, vol. 41, no. 8, pp. 1792-1802, Aug. 2006.

Ultra-wideband Pulse Radio:

- Tien-Ling Hsieh, P. Kinget, Ranjit Gharpurey, "An Approach to Interference Detection for Ultra Wideband Radio Systems", Fifth IEEE Dallas Circuits and Systems Workshop, pp. 91-94, Oct. 2006.
- F. Zhang and P. Kinget, "Low Power Programmable Gain CMOS Distributed LNA" IEEE Journal of Solid-State Circuits, vol. 41, no 6, pp. 1033-1043, June 2006.
- A. Jha, R. Gharpurey and P. Kinget, "Quadrature-DAC based pulse generation for UWB pulse radio transceivers" in Digest of Technical Papers IEEE International Symposium on Circuits and Systems, pp. 666-669, May 2006.

Injection-locking:

- G. Gangasani and P. Kinget, "A time-domain model for predicting the injection locking bandwidth of non-harmonic oscillators" in Transactions on Circuits and Systems II, pp. 1035-1038, Oct. 2006.
- G. Gangasani and P. Kinget, "Injection-Lock Dynamics in Non-Harmonic Oscillators" in Digest of Technical Papers IEEE International Symposium on Circuits and Systems, pp. 1675-1678, May 2006.

Device Mismatch:

- P. Kinget, "Device mismatch and Tradeoffs in the Design of Analog Circuits", IEEE Journal of Solid-State Circuits, vol. 40, no 6, pp. 1212-1224, June 2005.

Acknowledgments

- Collaborators:
 - Y. Tsvividis (Columbia), K. P. Pun (City Univ. Hong Kong), S. Chatterjee (now IIT Delhi), B. Soltanian (now LSI)
 - A. Balankutty, Y. Feng, A. Jha, J. Shen, N. Stanic, S. Yu, F. Zhang.
- Analog Devices, Bell Labs, Intel, NSF, Realtek, Silicon Labs, SRC for financial support.
- Europractice, Philips (now NXP) and UMC for fabrication support.

Thank you for your attention

Any Questions, contact:

kinget@ee.columbia.edu

<http://www.ee.columbia.edu/~kinget>