

# **DIGITAL CLOCK TESTING REPORT**


**Georgios Charitos (gc2662)**

**Srinidhi Srinivasan (ss4974)**


# Table of Contents

<b>1)Pin Diagram.....</b>	<b>2</b>
<b>2)Block Diagram.....</b>	<b>3</b>
<b>3)Testing.....</b>	<b>4</b>
<b>3.1)Power Supply to the Chip.....</b>	<b>4</b>
<b>3.2)1Hz Test Pin.....</b>	<b>5</b>
<b>3.3)Minutes MSD MSB.....</b>	<b>6</b>
<b>3.4)Enable Signals.....</b>	<b>8</b>
<b>3.5)7-segment display verification.....</b>	<b>10</b>
<b>3.6)Global Reset Verification.....</b>	<b>12</b>
<b>3.7)Setting Mode Verification.....</b>	<b>14</b>
<b>3.8)Crystal Oscillator Verification.....</b>	<b>15</b>
<b>4)PCB Testing.....</b>	<b>16</b>

# 1. Pin Diagram

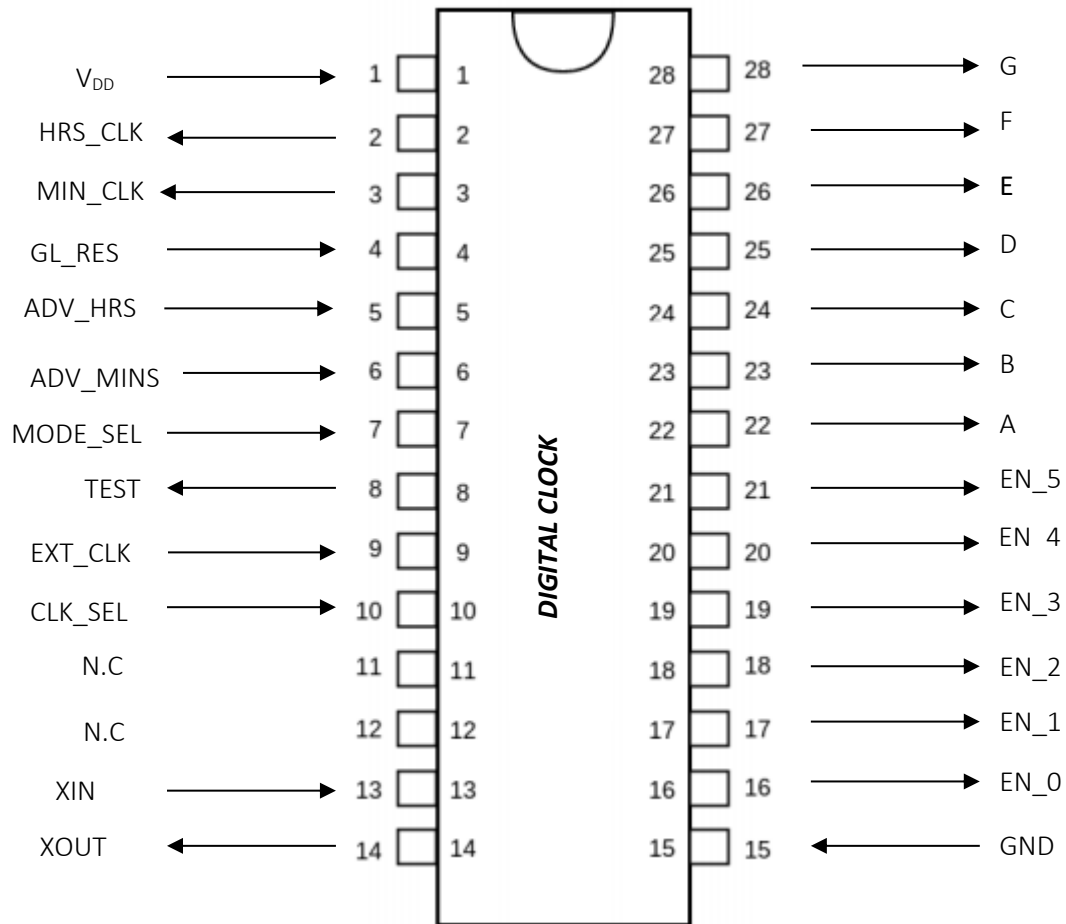

## 2. Block Diagram

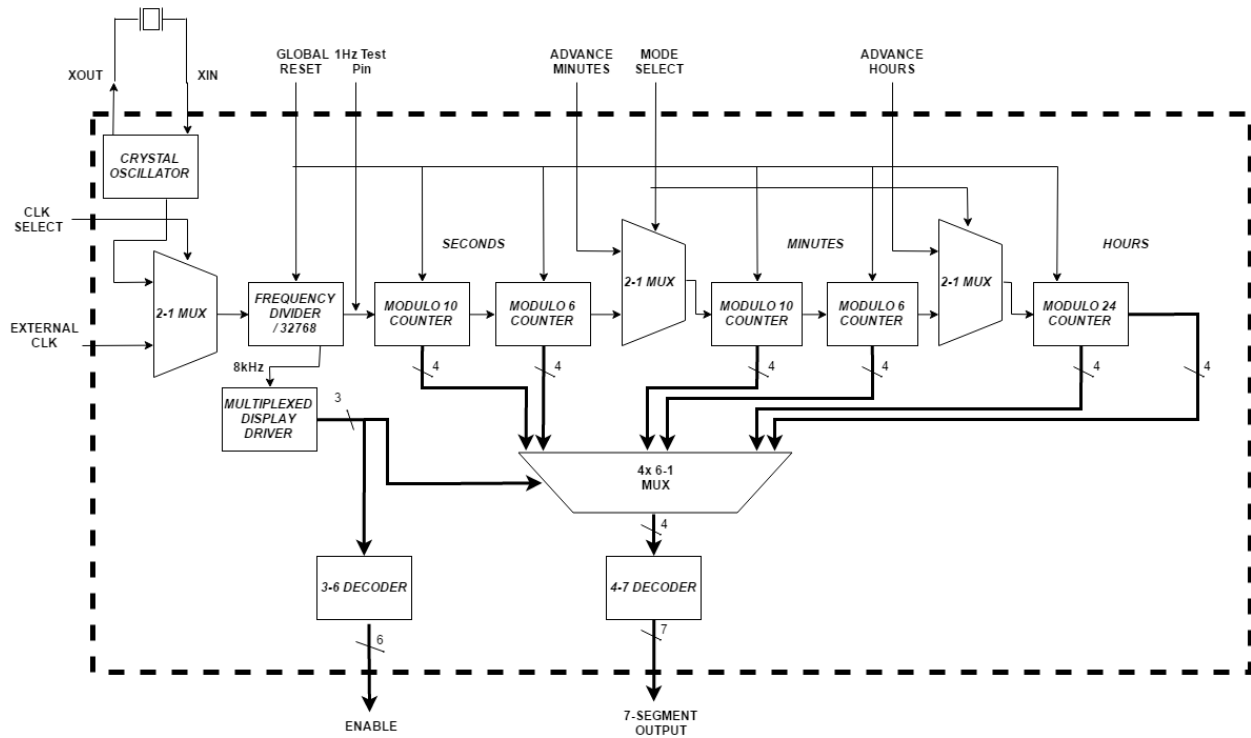

\* Dotted line represents chip boundary.

### 3. Testing



For the testing we will use  $V_{DD} = 1.2V$  as Power Supply, a Frequency Generator indicated as FG, an Oscilloscope indicated as Osc-CH# where CH# is the channel number and finally N.C. as No Connection.

#### 3.1 Power Supply to the chip

Before proceeding we first need to power up the chip and check for Power to Ground sorting:



We notice that no current is flowing between Power and Ground so we can proceed.


### 3.2 1Hz Test Pin

The first step for testing our chip is verifying the 1Hz frequency at the output of the frequency division chain comprised of 15 2-divider DFF's. In order to obtain desirable HHIGH and LOW voltage values, We will set the frequency generator as:


- Waveform Type: Square Wave
- Frequency: 32.768kHz
- Amplitude: 1.2V<sub>pp</sub>
- Offset: 0.6V
- Duty Cycle: 50%
- Output: High-Z

The pin connections must be:

Pin#	Pin Name	Connection	Pin#	Pin Name	Connection
1	V <sub>DD</sub>	V <sub>DD</sub>	15	GND	GND
2	HRS_CLK	N.C.	16	EN_0	N.C.
3	MIN_CLK	N.C.	17	EN_1	N.C.
4	GL_RES	GND	18	EN_2	N.C.
5	ADV_HRS	GND	19	EN_3	N.C.
6	ADV_MIN	GND	20	EN_4	N.C.
7	MODE_SEL	GND	21	EN_5	N.C.
8	1Hz_TEST	Osc-CH1	22	A	N.C.
9	EXT_CLK	F.G.	23	B	N.C.
10	CLK_SEL	V <sub>DD</sub>	24	C	N.C.
11	N.C.	N.C.	25	D	N.C.
12	N.C.	N.C.	26	E	N.C.
13	XIN	N.C.	27	F	N.C.
14	XOUT	N.C.	28	G	N.C.

 


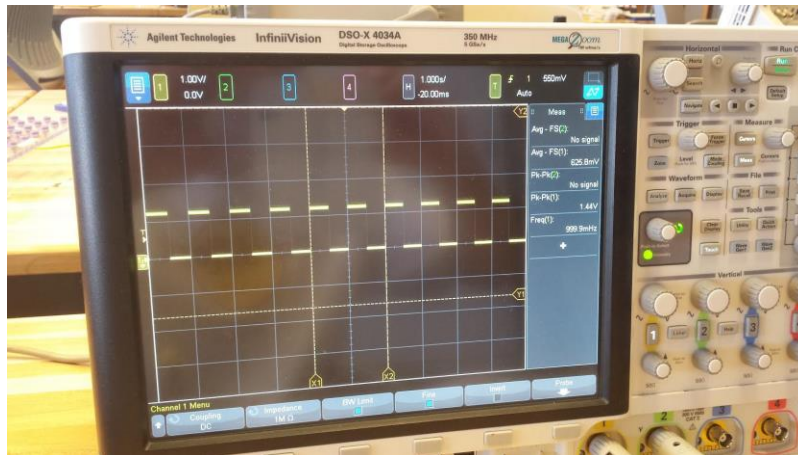Below we can see the 1Hz Output of the 1Hz\_TEST pin in the Oscilloscope.


 
### 3.3 Minutes MSD MSB

The next output we will test is the MIN\_CLK pin. This the inverted output is the MSB of the MSD of the Seconds:




This pin is asserts and de-asserts once every 60s. More specifically the truth table of the MSD is:

SECONDS	MSD	SECONDS	MIN_CLK
0	0	0-10	1
0	0	10-20	1
0	1	20-30	1
0	1	30-40	1
1	0	40-50	0
1	0	50-60	0

The Pin configuration is as follows:

Pin#	Pin Name	Connection	Pin#	Pin Name	Connection
1	V <sub>DD</sub>	V <sub>DD</sub>	15	GND	GND
2	HRS_CLK	N.C.	16	EN_0	N.C.
3	MIN_CLK	Osc-CH1	17	EN_1	N.C.
4	GL_RES	GND	18	EN_2	N.C.
5	ADV_HRS	GND	19	EN_3	N.C.
6	ADV_MIN	GND	20	EN_4	N.C.
7	MODE_SEL	GND	21	EN_5	N.C.
8	1Hz_TEST	N.C.	22	A	N.C.
9	EXT_CLK	F.G.	23	B	N.C.
10	CLK_SEL	V <sub>DD</sub>	24	C	N.C.
11	N.C.	N.C.	25	D	N.C.
12	N.C.	N.C.	26	E	N.C.
13	XIN	N.C.	27	F	N.C.
14	XOUT	N.C.	28	G	N.C.

 The result can be seen in the Oscilloscope:











### 3.4 Enable Signals

In order to view the EN\_5 signal that concerns the LSD of the seconds the connections must be as follows:

Pin#	Pin Name	Connection	Pin#	Pin Name	Connection
1	V <sub>DD</sub>	V <sub>DD</sub>	15	GND	GND
2	HRS_CLK	N.C.	16	EN_0	N.C.
3	MIN_CLK	N.C.	17	EN_1	N.C.
4	GL_RES	GND	18	EN_2	N.C.
5	ADV_HRS	GND	19	EN_3	N.C.
6	ADV_MIN	GND	20	EN_4	N.C.
7	MODE_SEL	GND	21	EN_5	Osc-CH1
8	1Hz_TEST	N.C.	22	A	N.C.
9	EXT_CLK	F.G.	23	B	N.C.
10	CLK_SEL	V <sub>DD</sub>	24	C	N.C.
11	N.C.	N.C.	25	D	N.C.
12	N.C.	N.C.	26	E	N.C.
13	XIN	N.C.	27	F	N.C.
14	XOUT	N.C.	28	G	N.C.

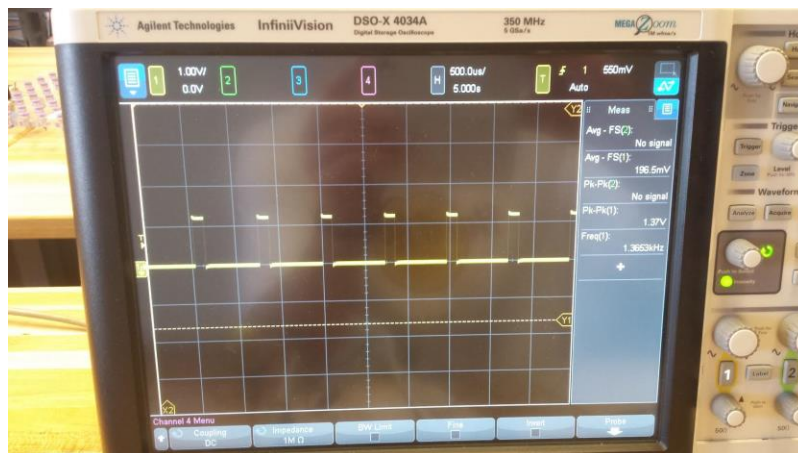

     Now, to verify that every enable signal is adjacent to the previews and the next we have to keep the oscilloscope channel 1 at EN\_5 and channel 2 at EN\_4, EN\_3, EN\_2, EN\_1, EN\_0 sequentially.



### 3.5 7-Segment LED Display Verification

To verify the 7-segments LED Display we will check the LSD of the seconds, which means outputting EN\_5 and simultaneously look at the E,F,G segments for 10s and check if they satisfy the truth table below:




Binary Inputs				Decoder Outputs							7 Segment Display Outputs
D	C	B	A	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	1
0	0	1	0	1	1	0	1	1	0	1	2
0	0	1	1	1	1	1	1	0	0	1	3
0	1	0	0	0	1	1	0	0	1	1	4
0	1	0	1	1	0	1	1	0	1	1	5
0	1	1	0	1	0	1	1	1	1	1	6
0	1	1	1	1	1	1	0	0	0	0	7
1	0	0	0	1	1	1	1	1	1	1	8
1	0	0	1	1	1	1	1	0	1	1	9


The pin connections are shown below:

Pin#	Pin Name	Connection	Pin#	Pin Name	Connection
1	V <sub>DD</sub>	V <sub>DD</sub>	15	GND	GND
2	HRS_CLK	N.C.	16	EN_0	N.C.
3	MIN_CLK	N.C.	17	EN_1	N.C.
4	GL_RES	GND	18	EN_2	N.C.
5	ADV_HRS	GND	19	EN_3	N.C.
6	ADV_MIN	GND	20	EN_4	N.C.
7	MODE_SEL	GND	21	EN_5	Osc-CH1
8	1Hz_TEST	N.C.	22	A	N.C.
9	EXT_CLK	F.G.	23	B	N.C.
10	CLK_SEL	V <sub>DD</sub>	24	C	N.C.
11	N.C.	N.C.	25	D	N.C.
12	N.C.	N.C.	26	E	Osc-CH2
13	XIN	N.C.	27	F	Osc-CH3
14	XOUT	N.C.	28	G	Osc-CH4



 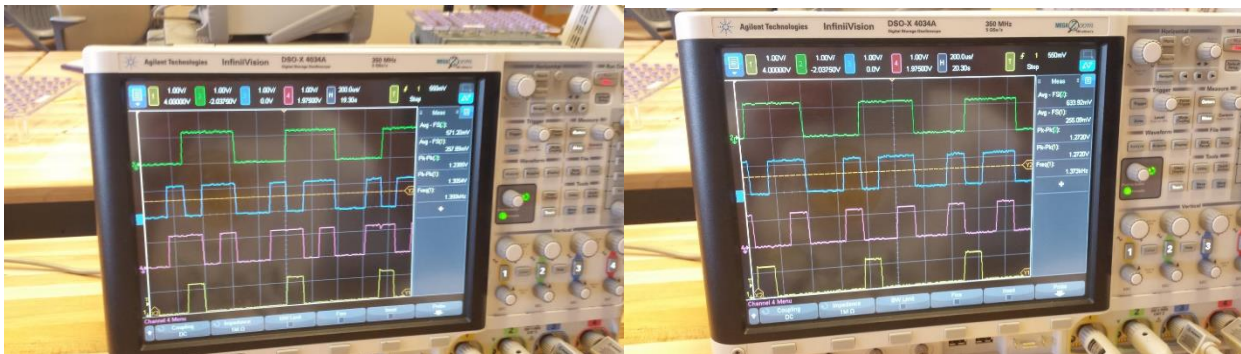 A 10 second run of the clock gave the outputs below:



 

### 3.6 Global Reset Verification

To verify the GL\_RES function, we will use another frequency generator(F.G.-2) and give a 0.1Hz pulse as input to the GL\_RES:

- Waveform Type: Pulse
- Frequency: 0.1Hz
- Amplitude: 1.2V<sub>pp</sub>
- Offset: 0.6V
- Delay: 1s
- Output: High-Z






We need to connect the pins as shown:

Pin#	Pin Name	Connection	Pin#	Pin Name	Connection
1	V <sub>DD</sub>	V <sub>DD</sub>	15	GND	GND
2	HRS_CLK	N.C.	16	EN_0	N.C.
3	MIN_CLK	N.C.	17	EN_1	N.C.
4	GL_RES	F.G.-2	18	EN_2	N.C.
5	ADV_HRS	GND	19	EN_3	N.C.
6	ADV_MIN	GND	20	EN_4	N.C.
7	MODE_SEL	GND	21	EN_5	N.C.
8	1Hz_TEST	Osc-CH1	22	A	N.C.
9	EXT_CLK	F.G.-1	23	B	N.C.
10	CLK_SEL	V <sub>DD</sub>	24	C	N.C.
11	N.C.	N.C.	25	D	N.C.
12	N.C.	N.C.	26	E	N.C.
13	XIN	N.C.	27	F	N.C.
14	XOUT	N.C.	28	G	N.C.

 The result on the 1Hz output is shown below:



### 3.7 Setting Mode Verification

The setting mode will be tested by setting the MODE\_SEL at the setting mode, setting a 1Hz input to the ADV\_MIN and looking at EN\_3 and C, D, E segments. The pin connection is shown below:



Pin#	Pin Name	Connection	Pin#	Pin Name	Connection
1	V <sub>DD</sub>	V <sub>DD</sub>	15	GND	GND
2	HRS_CLK	N.C.	16	EN_0	N.C.
3	MIN_CLK	N.C.	17	EN_1	N.C.
4	GL_RES	GND	18	EN_2	N.C.
5	ADV_HRS	GND	19	EN_3	Osc-CH1
6	ADV_MIN	F.G.-2	20	EN_4	N.C.
7	MODE_SEL	V <sub>DD</sub>	21	EN_5	N.C.
8	1Hz_TEST	N.C.	22	A	N.C.
9	EXT_CLK	F.G.-1	23	B	N.C.
10	CLK_SEL	V <sub>DD</sub>	24	C	Osc-CH2
11	N.C.	N.C.	25	D	Osc-CH3
12	N.C.	N.C.	26	E	Osc-CH4
13	XIN	N.C.	27	F	N.C.
14	XOUT	N.C.	28	G	N.C.

Again, we run a simulation for 10 seconds and check the C, D, E sequence to be according to the 7-segment truth table:


  
### 3.8 Crystal Oscillator Verification:

Finally, we test the crystal oscillator. We want to see the 32.768kHz frequency and 1.2 V<sub>pp</sub> offset by 0.6V in the Oscillator output XIN and the 1Hz test pin having the 1Hz frequency signal:





## 4. PCB Testing

After verifying the chip's operation, we started testing it with the PCB:

- Power Circuitry Test

Before plugging the chip, we measured the voltage at all crucial test-points like the regulator outputs. We did it first with the 9V battery source and then with the 5V USB.

 


Fig. 5.4: Power Circuitry Test

- Led Display Test

Next we tested the led displays by setting proper voltage values to the A-G segments and verifying the output of the LEDs.

- External Frequency Generator Test

At this point we feel confident enough to place our chip on the PCB. Our first function test included the external frequency generator. By setting the appropriate values to our input pins, we could see the LED digits showing the proper output.

- Oscillator Test

Next we tested the crystal with the in-chip oscillator. Also we tested the external oscillator source as well.

 


Fig. 5.5: Oscillator Test Frequency

 


Fig. 5.6: Testing of PCB with chip mounted

 


Fig. 5.6: Final Product operation